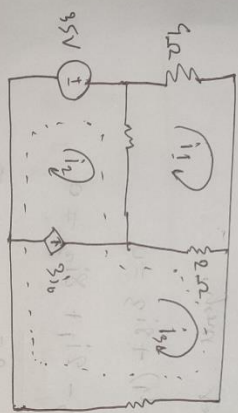


Nam: Khan Nd Shafatul Islam
 Student Id: 20182801320

Ans: 1

Let's get the mesh currents that are labeled

as shown below:



Now, I'm going to apply Kirchhoff's law (voltage),
 the algebraic sum of all voltages
 around a closed path (or loop) is zero.
 For mesh 1, we get accordingly,

②

$$4i_1 + 2(i_1 - i_3) + 10(i_1 - i_2) = 0$$

$$\Rightarrow 4i_1 + 2i_1 - 2i_3 + 10i_1 - 10i_2 = 0$$

$$\Rightarrow 16i_1 - 10i_2 - 2i_3 = 0$$

$$\Rightarrow 8i_1 - 5i_2 - i_3 = 0 \quad \text{--- (i)}$$

Applying Kirchhoff's voltage law to mesh 2 and

$$\text{mesh 3 formed super mesh,}$$

$$-35 + 10(i_2 - i_1) + 2(i_3 - i_1) + 8i_3 = 0$$

$$\Rightarrow -35 + 10i_2 - 10i_1 + 2i_3 - 2i_1 + 8i_3 = 0$$


$$\Rightarrow -12i_1 + 10i_2 + 10i_3 = 35 \quad \text{--- (ii)}$$

Applying Kirchhoff's current law at Node A:

$$3i_0 = i_3 - i_2$$

$$\text{But } i_0 = 11$$

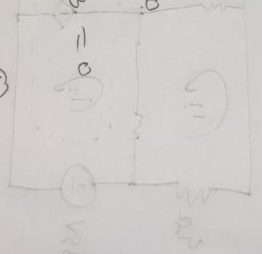Substituting i_1 for i_0 in ~~question~~ equation



(3)

$$8i_1 = i_3 - i_2$$

$$\Rightarrow 8i_1 = i_3 - i_2$$

$$\Rightarrow 9i_1 + i_2 - i_3 = 0 \quad \text{--- (iii)}$$

Subtracting (iii) from (i)

$$8i_1 - 5i_2 - i_3 = 0$$

$$9i_1 + i_2 - i_3 = 0$$

$$5i_1 - 6i_2 = 0$$

$$\Rightarrow 5i_1 - 6i_2 = 0 \quad \text{--- (iv)}$$

$$(i) \times 10 + (ii) \Rightarrow$$

$$80i_1 - 50i_2 - 10i_3 = 0$$

$$-12i_1 + 10i_2 + 10i_3 = 35$$

$$\Rightarrow 68i_1 - 40i_2 = 35 \quad \text{--- (v)}$$

Q4 Solving (iv) and (v) \Rightarrow

$$i_1 = 1.01 A$$

$$i_2 = .84 A$$

~~find~~ finding the value of i_0 ^{(if mark (iii) get satisfied)}

$$i_0 = i_1$$

$$= 1.01 A$$

\therefore current


$$i_0 = 1.01 A$$

$$\underline{\underline{Ans: 1.01 A}}$$

Ans: 2

from fig, the nodes c, t are at the same point. Hence, redraw the fig \rightarrow

5

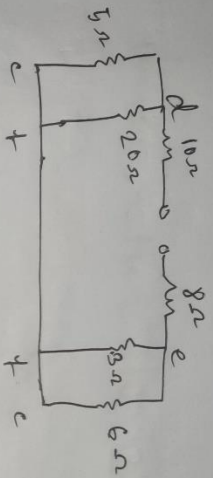

We can see 20Ω , 5Ω and 6Ω , 3Ω are parallel.

Calculating the value of the parallel equivalent resistance, R_{eq} , for 20Ω , 5Ω ,

$$R_{eq} = 20\Omega \parallel 5\Omega$$

$$= \frac{20\Omega(5\Omega)}{20\Omega + 5\Omega}$$

$$= \frac{100}{25} \Omega = 4\Omega$$

$$\therefore R_{eq} = 4\Omega$$


Calculating the value of resistance R_{eq} for 6Ω , 3Ω .

(6)

$$R_{eq} = 6 \parallel 13 \Omega$$

$$= \frac{6 \Omega (13 \Omega)}{6 \Omega + 13 \Omega}$$

$$= \frac{18}{9} \Omega = 2 \Omega$$

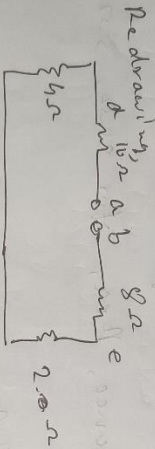


From above, $10 \Omega, 8 \Omega, 2 \Omega, 4 \Omega$ are in series.

Calculating R_{ab} for above,

$$R_{ab} = 10 \Omega + 8 \Omega + 2 \Omega + 4 \Omega$$

$$= 24 \Omega$$

Again, Redrawing,

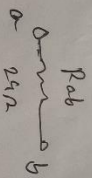

(7)

④

Therefore, the value of equivalent $R_{ab} = 24\Omega$

Ans. 4

The circuit is a non-inverting amplifier.

Writing the expression for output voltage:

$$V_o = \left(1 + \frac{R_F}{R_i}\right) V_i$$

Substituting $50k\Omega$ for R_F , $10k\Omega$ for R_i

and $4mV$ for V_i

$$V_o = \left(1 + \frac{50k\Omega}{10k\Omega}\right) (4mV)$$

$$\Rightarrow (1+5) (4mV)$$

$$\Rightarrow (6) (4mV)$$

$$\Rightarrow 24mV$$

⑤

Here, a resistor combination is connected as load, to the non-inverting amplifier. The $60k\Omega$ and $30k\Omega$ are in parallel.

$$R_{eq} = \frac{(60k\Omega)(30k\Omega)}{60k\Omega + 30k\Omega}$$

$$= \frac{1800k\Omega}{90}$$

$$= 20k\Omega$$

It's in series combination with the parallel combination

$$\therefore R_{Total} R_T \text{ is } 40k\Omega$$

The current through $20k\Omega$ is

$$I_R = \frac{V_{o1}}{R_T}$$

Subbing $24mV$ for V_{o1} and $40k\Omega$ for

③

$$i_{in} = \frac{24 \text{ mV}}{40 \text{ k}\Omega}$$

$$= 6 \times 10^{-6} = \underline{\underline{6 \mu\text{A}}}$$

Voltage across the $60 \text{ k}\Omega$

$$P_D = \frac{V_o^2}{60 \text{ k}\Omega}$$

Substituting 12 mV for V_o

$$P_D = \frac{(12 \times 10^{-3})^2}{60 \text{ k}\Omega}$$

$$= \frac{144 \times 10^{-6}}{60000} = 24 \times 10^{-10} = \underline{\underline{2.4 \text{ nW}}}$$

\therefore Power dissipated in $60 \text{ k}\Omega$ is 2.4 nW

(Ans)

10

Ans: 2

Apply Kirchhoff's current law at node v_o .

$$\frac{v_o}{10k} + \frac{v_o}{40k} + \frac{v_o - 1}{22k} = 0$$

$$\Rightarrow \frac{v_o}{10} + \frac{v_o}{40} + \frac{v_o - 1}{22} = 0$$

$$\Rightarrow 44v_o + 11v_o + 20v_o - 20 = 0$$

$$\Rightarrow 75v_o = 20$$

$$\Rightarrow v_o = \frac{20}{75} = \frac{4}{15} \text{ V}$$

$$44v_o + 11v_o + 20v_o - 20 = 0$$

$$75v_o = 20$$

$$v_o = \frac{20}{75} = \frac{4}{15} \text{ V}$$

⑦

Name to Med IV. Sisof

$$\frac{V_0 - 1}{22k} + 0.003V_0 + i_0 = \frac{1}{30k}$$

$$\Rightarrow \frac{V_0 - 1}{22k} + 3V_0 + 1000i_0 = \frac{1}{30k} + \frac{V}{1001}$$

$$\Rightarrow 30V_0 - 30 + 198V_0 + 660000i_0 = 22$$

$$\Rightarrow 2010V_0 + 660000i_0 = 52$$

Subbing $V_0 = \frac{4}{15} V$ in the eq.

$$2010 \left(\frac{4}{15} \right) + 660000i_0 = 52$$

$$\Rightarrow 536 + 660000i_0 = 52$$

$$\Rightarrow 660000i_0 = -484$$


$$\Rightarrow i_0 = -733 \mu A$$

Calculate the Thevenin resistance.

12

$$R_{Th} = \frac{1}{I_0} = \frac{1}{-7.33 \times 10^{-6}} = -1,3636 k\Omega$$

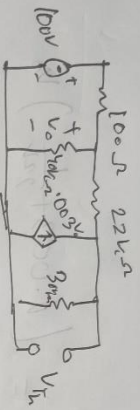Now circuit to calculate Thevenin voltage.



At Node V_0 Kirchhoff's law,

$$\frac{V_0 - 100}{10k} + \frac{V_0}{40k} + \frac{V_0 - V_{Th}}{22k} = 0$$

$$\Rightarrow \frac{V_0}{10} + \frac{V_0}{40} + \frac{V_0 - V_{Th}}{22} = \frac{100}{10}$$

$$\Rightarrow \frac{44V_0 + 11V_0 + 20V_0 - 20V_{Th}}{440} = \frac{44000}{440}$$

$$\Rightarrow 75V_0 - 20V_{Th} = 4400$$

$$\Rightarrow 75V_0 = 20V_{Th} + 4400$$

$$\Rightarrow V_0 = 0.2667 V_{Th} + 58.67 \quad \text{--- (1)}$$

(13)

Apply Kirchhoff's law at V_n .

$$\frac{V_n - V_o}{22k} + \frac{V_n}{30k} = 0.003k_o$$

$$\Rightarrow \left(\frac{1}{22k} + \frac{1}{30k} \right) V_n = \left(0.003 + \frac{1}{24} \right) V_o$$

$$\Rightarrow \left(\frac{1}{22} + \frac{1}{30} \right) V_n = \left(3 + \frac{1}{22} \right) V_o$$

$$\Rightarrow \left(\frac{30+22}{660} \right) V_n = \left(\frac{66+1}{22} \right) V_o$$

$$\Rightarrow V_n = \left(\frac{67}{22} \right) \left(\frac{660}{52} \right) V_o$$

$$\Rightarrow 36.65 V_o$$

(14)

(21)

Ans: 10

Resonant frequency:

The resonant frequency ω is
for a series RLC circuit is

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(40 \times 10^{-3})(1 \times 10^{-6})}}$$

(15)

$$= 5 \text{ k} \Omega$$

Impedance at resonance,

The impedance of a series RLC network is

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

At $\omega = \omega_0$

Since, the impedance of a series

RLC circuit is purely resistive at

resonant frequency,

$$Z_{\omega_0} = R$$

$$\Rightarrow Z_{\omega_0} = 1 \text{ k}\Omega$$

(Ans)

Q3

Ans: 7

For $t < 0$, the inductor acts as a short circuit to dc and the circuit becomes what shown below. Applying KVL to left loop of the circuit shown

$$4i_0 - 2i_0 + 24 \Rightarrow i_0 = 24 \text{ A}$$

Applying KVL to the 2nd mesh given,

$$i(0) = \frac{4i_0}{2} = \frac{4 \cdot 24}{2} = 48 \text{ A}$$

For $t > 0$, the switch is moved so that the current i_0 becomes 0 to zero. Thus, the dependent voltage source ($4i_0$) can be replaced with

(14)

a short circuit and circuit shown below become a source free RL circuit. Time constant,


$$\tau = \frac{L}{R} = \frac{.5}{2} = \frac{1}{4} \text{ s}$$


inductor current for $t > 0$ is

$$i(t) = i(0) e^{-t/\tau} = 48 e^{-4t} \text{ A}$$


Thus the inductor current is
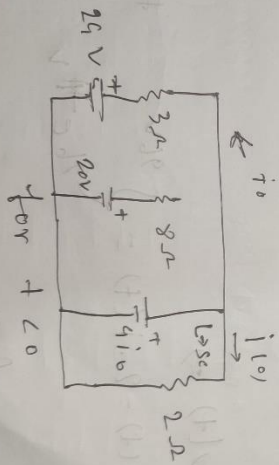
$$i(t) = \begin{cases} 48 \text{ A} & t < 0 \\ 48 e^{-4t} \text{ A} & t > 0 \end{cases}$$



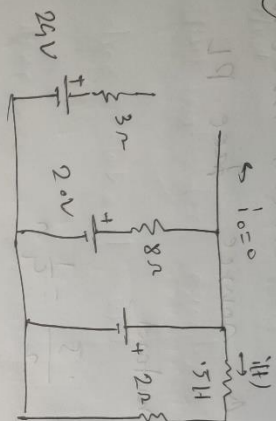

for $t > 0$

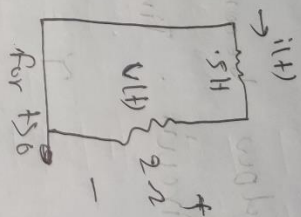

Applying Ohm's law to the 2Ω resistor gives

$$V(t) = 2 \cdot i(t)$$

$$\begin{cases} 96V & t < 0 \\ 96e^{-4t}V & t > 0 \end{cases}$$

voltage $V(t) \Rightarrow$

$$v(t) = 2 \cdot i(t) = \begin{cases} 96V & t < 0 \\ 96e^{-4t}V & t > 0 \end{cases}$$

(Answer)

19

Ans:


To find Z_{Th} remove Z_L and open circuit $5\angle 90^\circ$ (current source) short circuit $6\angle 0^\circ$ (voltage source)

$$40\Omega \parallel 40\Omega$$

$$= \frac{40 \times 40}{40 + 40} = 20\Omega$$

$$-j16 \parallel 80\Omega = \frac{80 \times -j16}{80 - j16}$$

$$= 1.23 - j9.846\Omega$$

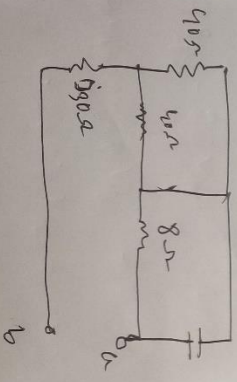

(90)

20Ω and $1.13 - j9.846\Omega$ are in

series with $j30$ given $Z_{ab} =$

$$Z_{ab} = 20 + 1.13 - j9.846 + j30 \text{ (Hussein)}$$
$$= 21.13 + j20.15\Omega$$


For maximum power transfer

$$Z_1 = \text{conjugate}(Z_{ab})$$

$$Z_1 = 21.13$$

$$Z_1 = 21.13 - j20.15 \text{ (Hussein)}$$

(Ans)

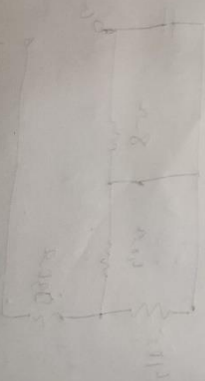

(21)

Ans: $\frac{6}{100} = \frac{100}{100} + \frac{100}{100}$

Here, $4\mu F$ is in series with $12\mu F$

$$\frac{(4 \times 12)}{4 + 12} = 3\mu F$$

And $3\mu F$ is in parallel with $3\mu F$

given.

$$3\mu F + 3\mu F = 6\mu F \text{ (overall)}$$

Now, $6\mu F$ is in series with $6\mu F$

$$\frac{6 \times 6}{6 + 6} = 3\mu F \text{ (ult)}$$

And, $3\mu F$ is in parallel with

$2\mu F$ given.

(Q2)

$$2 \mu F + 2 \mu F = 5 \mu F$$

And, $5 \mu F$ in in series with $5 \mu F$

given,

$$\frac{5 \times 5}{5+5} = 2.5 \mu F$$

Hence, $C_{eq} = 2.5 \mu F$

\therefore equivalent capacitance of terminal

$$A-B \text{ is } \underline{2.5 \mu F}$$

(Ans)

(62)

Ans. 4:5

$$V_1 = 6I_1 - j4I_2$$

$$V_2 = -j4I_1 + 8I_2$$

$$2 \angle 36^\circ = 2\dot{I}_1 + 4$$

$$V_2 = 0$$

Now,

$$\dot{I}_1 = 0.2 \angle 30^\circ \text{ A}$$

$$\dot{I}_2 = 0.1 \angle 120^\circ \text{ A}$$

$$\therefore \dot{I}_1 = 0.2 \text{ A}$$

$$I_2 = 0.1 \text{ A}$$

(Ans)