
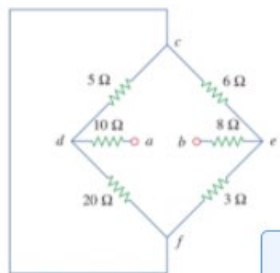
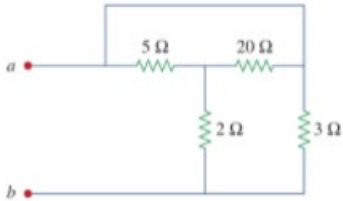


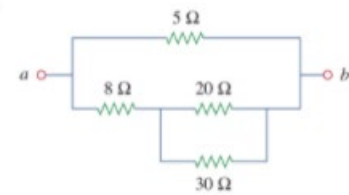3. For the circuits , obtain the equivalent resistance at terminals a-b.



Answer

Answer No 3

1st figure answer:

$$(a) \quad R_{ab} = 5 \parallel (8 + 20 \parallel 30) = 5 \parallel (8 + 12) = \frac{5 \times 20}{25} = \underline{4 \Omega}$$


$$(b) \quad R_{ab} = 2 + 4 \parallel (5 + 3) \parallel 8 + 5 \parallel 10 \parallel 4 = 2 + 4 \parallel 4 + 5 \parallel 2.857 = 2 + 2 + 1.8181 = \underline{5.818 \Omega}$$

2nd figure answer:

3rd figure answer:


$$5 \parallel 20 = \frac{5 \times 20}{25} = 4 \Omega$$
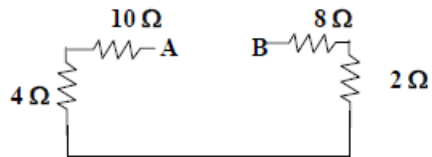
$$6 \parallel 3 = \frac{6 \times 3}{9} = 2 \Omega$$




$$R_{ab} = 10 + 4 + 2 + 8 = \underline{\underline{24 \Omega}}$$

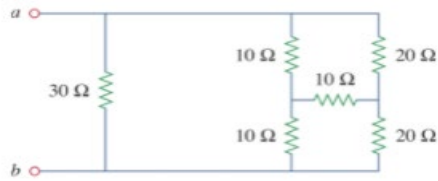4. Obtain the equivalent resistance at the terminals a-b for each of the circuits.



(a)

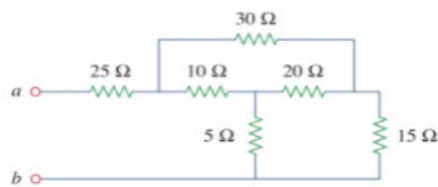


(b)

Answer No 4

$$(a) \quad 30 \parallel 30 = 15 \Omega \text{ and } 30 \parallel 20 = 30 \times 20 / (50) = 12 \Omega$$
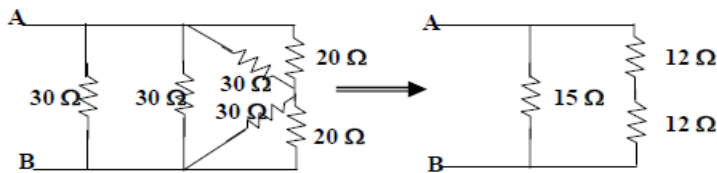
$$R_{ab} = 15 \parallel (12 + 12) = 15 \times 24 / (39) = \underline{9.231 \Omega}$$



(b) Converting the T-subnetwork into its equivalent Δ network gives

$$R_{a'b'} = 10 \times 20 + 20 \times 5 + 5 \times 10 / (5) = 350 / (5) = 70 \Omega$$

$$R_{b'c'} = 350 / (10) = 35 \Omega, R_{a'c'} = 350 / (20) = 17.5 \Omega$$

$$\text{Also } 30 \parallel 70 = 30 \times 70 / (100) = 21 \Omega \text{ and } 35 / (15) = 35 \times 15 / (50) = 10.5$$

$$R_{ab} = 25 + 17.5 \parallel (21 + 10.5) = 25 + 17.5 \parallel 31.5$$

$$R_{ab} = \underline{36.25 \Omega}$$

