


Circuit Analysis Final

25-Jun-21

Name: Tafsir Mubtasim Mahmood
ID: 2019380179

Class: V08M12065

Ans to the Q. No. 1

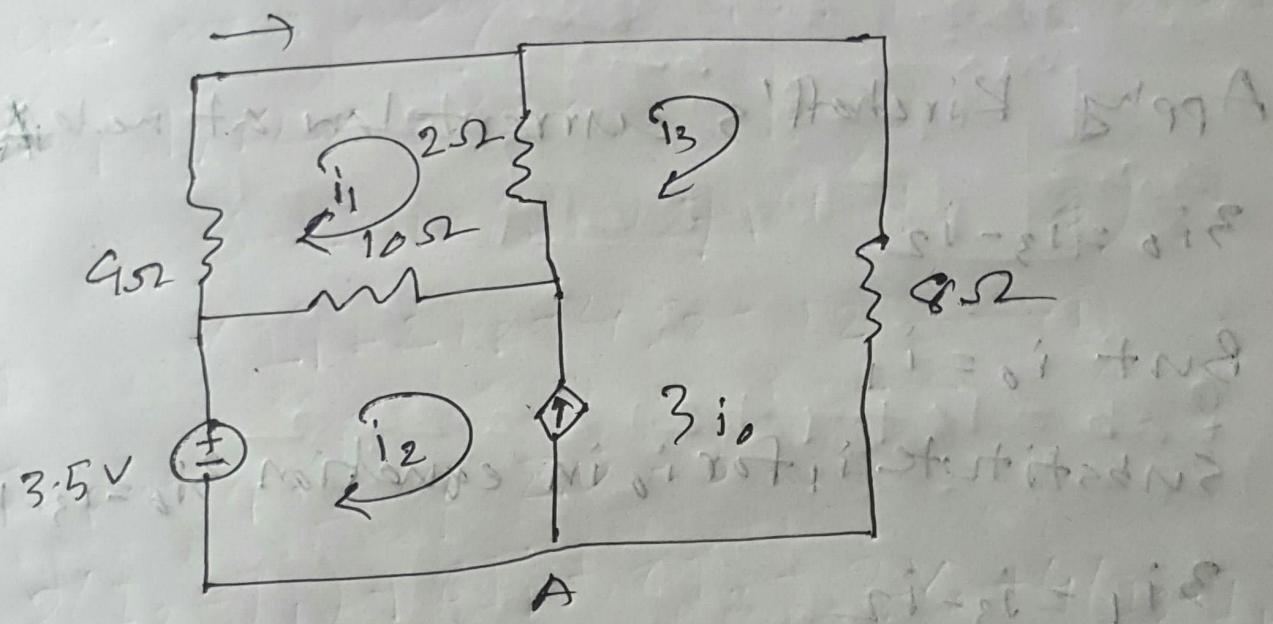

For mesh 1,

$$4i_1 + 2(i_1 - i_3) + 10(i_1 - i_2) = 0$$

$$\Rightarrow 4i_1 + 2i_1 - 2i_3 + 10i_1 - 10i_2 = 0$$

$$\textcircled{2} \quad 16i_1 - 10i_2 - 2i_3 = 0$$

$$\textcircled{3} \quad 8i_1 - 5i_2 - i_3 = 0$$

The meshes 2 and 3 form a super mesh,

$$-35 + 10(i_2 - i_1) + 8i_3 = 0$$

$$-35 + 10i_2 - 10i_1 + 2i_3 - 2i_1 + 8i_3 = 0$$

$$-12i_1 + 10i_2 + 10i_3 = 35 \quad \text{--- (2)}$$

Applying Kirchoff's current law at node A,

$$3i_o = i_3 - i_2$$

$$\text{But } i_o = i_1$$

Substitute i_1 for i_o in equation $3i_o = i_3 - i_2$

$$3i_1 = i_3 - i_2$$

$$3i_1 + i_2 - i_3 = 0 \quad \text{--- (3)}$$

Subtract equation (3) from (2)

$$8i_1 - 5i_2 - i_3 = 0$$

$$3i_1 + i_2 - i_3 = 0$$

$$\underline{5i_1 - 6i_2 = 0} \quad \text{--- (4)}$$

Multiply equation (1) by 10 and add it to equation (2)

$$80i_1 - 50i_2 - 10i_3 = 0$$

$$-12i_1 + 10i_2 + 10i_3 = 35$$

$$68i_1 - 40i_2 = 35 \quad (5)$$

Solve equation (4) and (5)

$$i_1 = 1.01 \text{ A}$$

$$i_2 = 0.84 \text{ A}$$


Determine the value of i_o ,

$$i_o = i_1$$

$$= 1.01 \text{ A}$$

Therefore the current i_o is 1.01 A

Ans. to the Q. No. 2

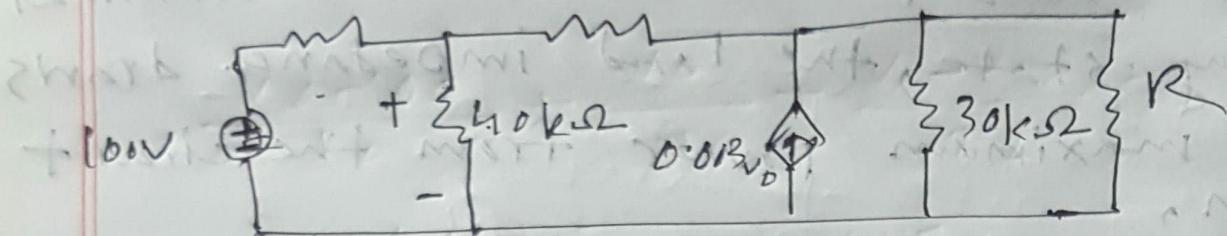

First we find R_{TH} .

Applying KCL to node (v_o) gives,

$$I_t + 6v_o = \frac{V_t}{30} + \frac{V_t - v_o}{22}$$

$$I_t = 0.6788V_t - 6.05v_o \quad \text{--- (1)}$$

Applying KCL to node (v_i) gives,

$$\frac{v_o}{10} + \frac{v_o}{40} + \frac{v_o - V_t}{22} = 0$$

$$0.1705v_o = 0.0455V_t \quad \text{--- (2)}$$

$$v_o = 0.2667V_t \quad \text{--- (2)}$$

Substituting eq(2) into eq(3)


~~$I_t = I_t = I_t = 0.0788 V_t - 6.05 \cdot (0.2667 V_t)$~~

~~$I_t = I_t = I_t = 0.0788 V_t - 6.05 \cdot (0.2667 V_t) =$~~

(1) $\rightarrow v_t = 11.7 V$

 $-1.535 V_t$

$\therefore R_{Th} = \left| \frac{V_t}{I_t} \right| = 651.58 \Omega$

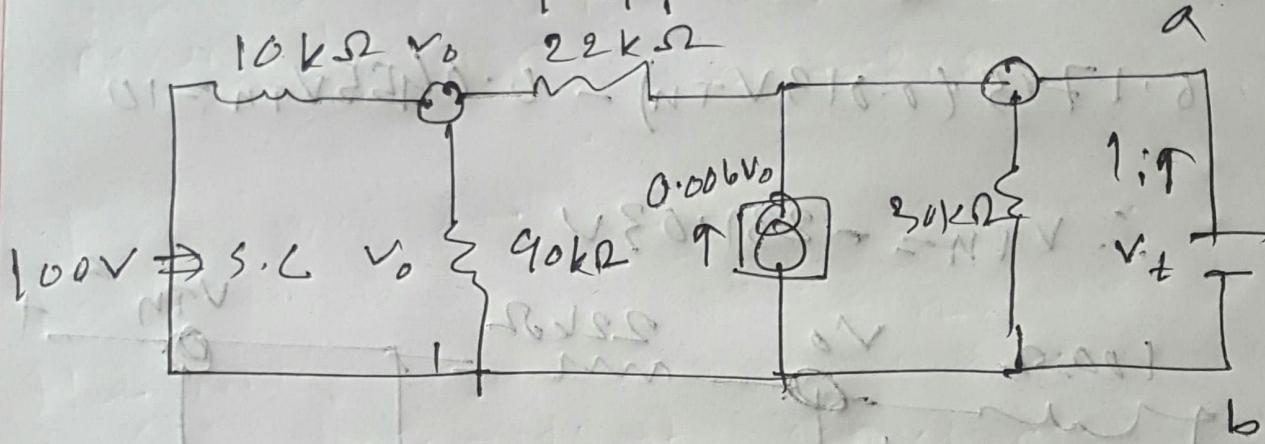

To find V_{Th} consider the circuit shown below,

Applying KCL to node (V_{Th}) gives

$6V_o = \frac{V_{Th}}{30} + \frac{V_{Th} - V_o}{22}$

$0.6788 V_{Th} = 6.095 V_o$

$\frac{V_o}{V_{Th}} = 0.013 \quad \text{--- (3)}$

Applying KCL at node (V_o)


$$\frac{V_o - 10}{10} + \frac{V_o}{90} + \frac{V_o - V_{Th}}{22k\Omega} = 0$$

$$6.1705V_o - 6.0455V_{Th} = 10 \quad (1)$$

Substituting Eq(1) into Eq2.

$$6.1705(0.013V_{Th}) - 6.0455V_{Th} = 10$$

$$\therefore V_{Th} = -231.03V$$

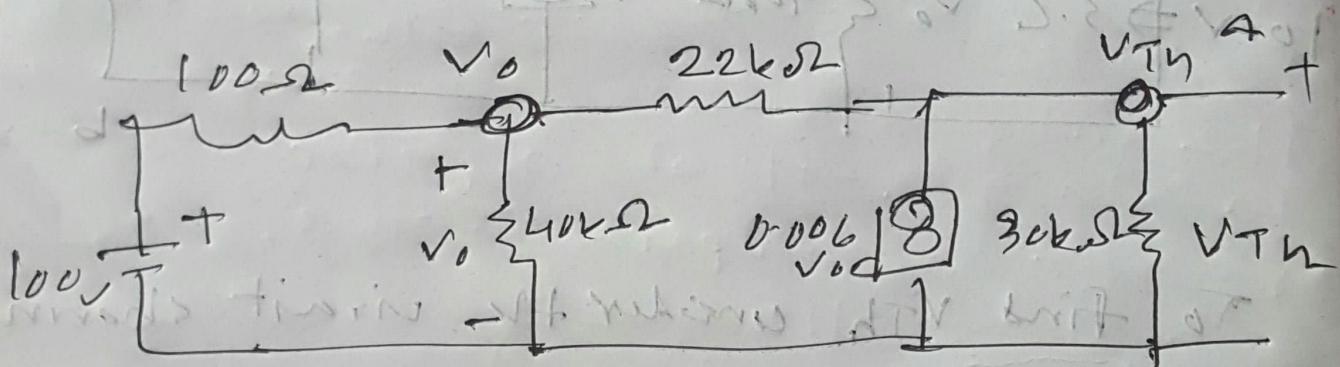

using (a) v (b) show of 10% principle

Finally, maximum power transfer

$$R = R_{Th} = 651.58\Omega$$

so the maximum power is


$$P_{max} = \frac{V_{Th}^2}{4R} = \frac{(-231.03)^2}{4 \cdot 651.58}$$

$$= 20.48W$$

Ans. to the Q. No. 3


$$5 \parallel 20 = \frac{5 \times 20}{25} = 4\Omega$$
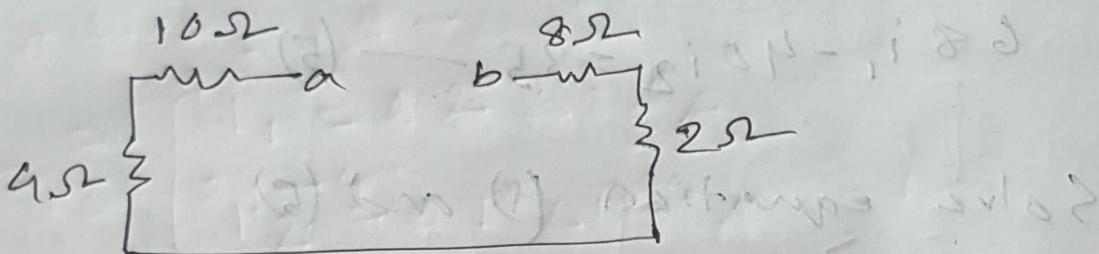
$$6 \parallel 3 = \frac{6 \times 3}{9} = 2\Omega$$



$$R_{ab} = 10 + 4 + 2 + 8 = 24\Omega$$

Ans. to the Q.No.7

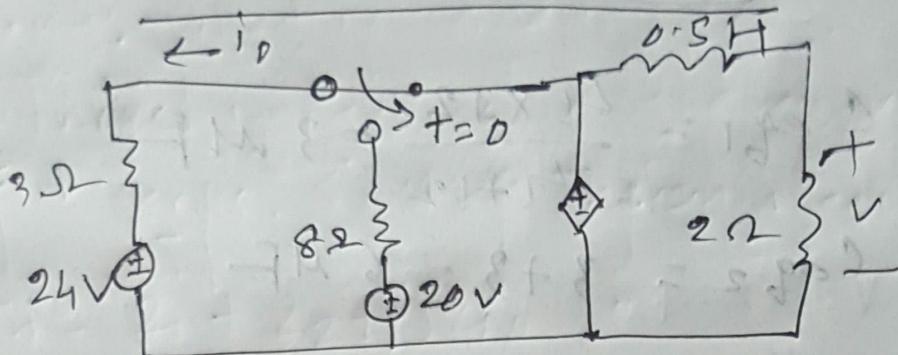

For $t < 0$,

$$3i_o + 24 - 4i_o = 0 \rightarrow i_o = 24$$

$$v(t) = 4i_o = 96V \quad i = \frac{v}{2} = 48A$$

For $t > 0$,

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-tr}$$

$$i(0) = 48, \quad i(\infty) = 0$$

$$R_{th} = 2\Omega, \quad T = \frac{L}{R_{th}} = \frac{0.5}{2} = \frac{1}{4}$$

$$i(t) = (48)e^{-4t}$$

$$v(t) = 2i(t) = 96e^{-4t} u(t) V$$

Ans. to the Q. No. 4


$$U^+ = U^- = 4 \text{ mV}$$

$$\therefore V_{o1} = 4 \times \left(1 + \frac{50}{10} \right) = 24 \text{ mV}$$

$$\begin{aligned}\therefore V_o &= \frac{V_{o1}}{20 + 60/140} \times (60/1130) \\ &= 1.2 \text{ mV}\end{aligned}$$

$$i_x = \frac{24 - 1.2}{20} = 0.6 \text{ mA}$$
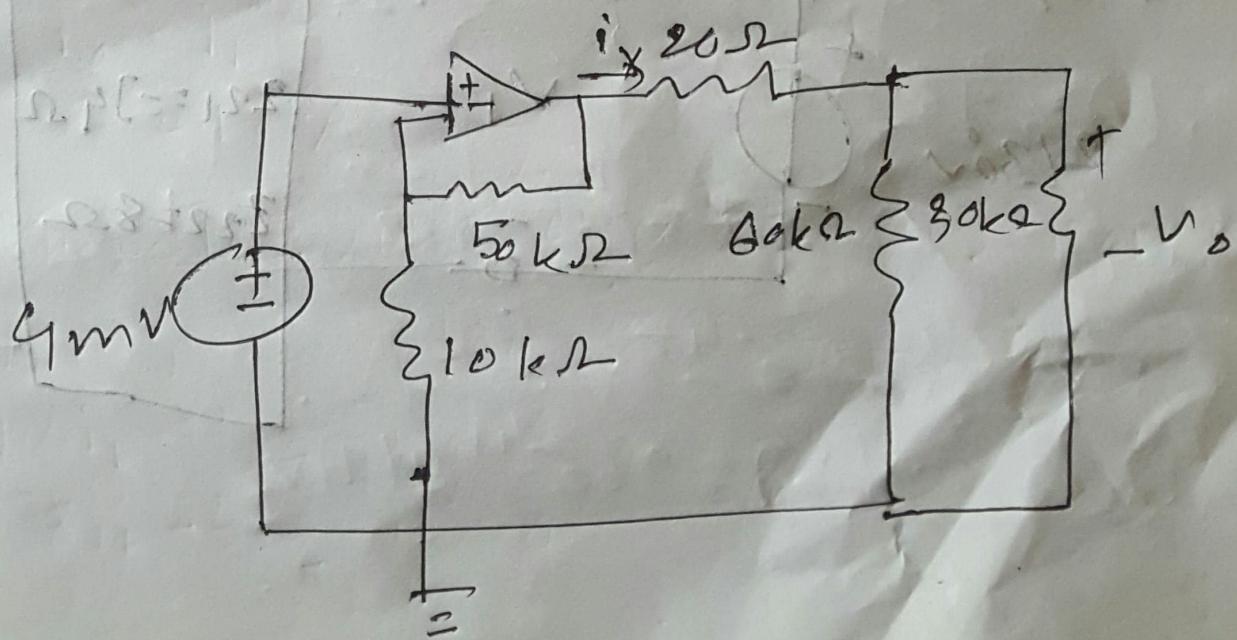
$$P_1 = \frac{U^2}{R} = 2.4 \times 10^{-9} \text{ W}$$




Ans. to the Q: No. 5

$$2[30^\circ - \underline{Z}]_1 = 6i_1 - j4i_2$$

$$\Rightarrow 0 = -j4i_1 + 8i_2$$
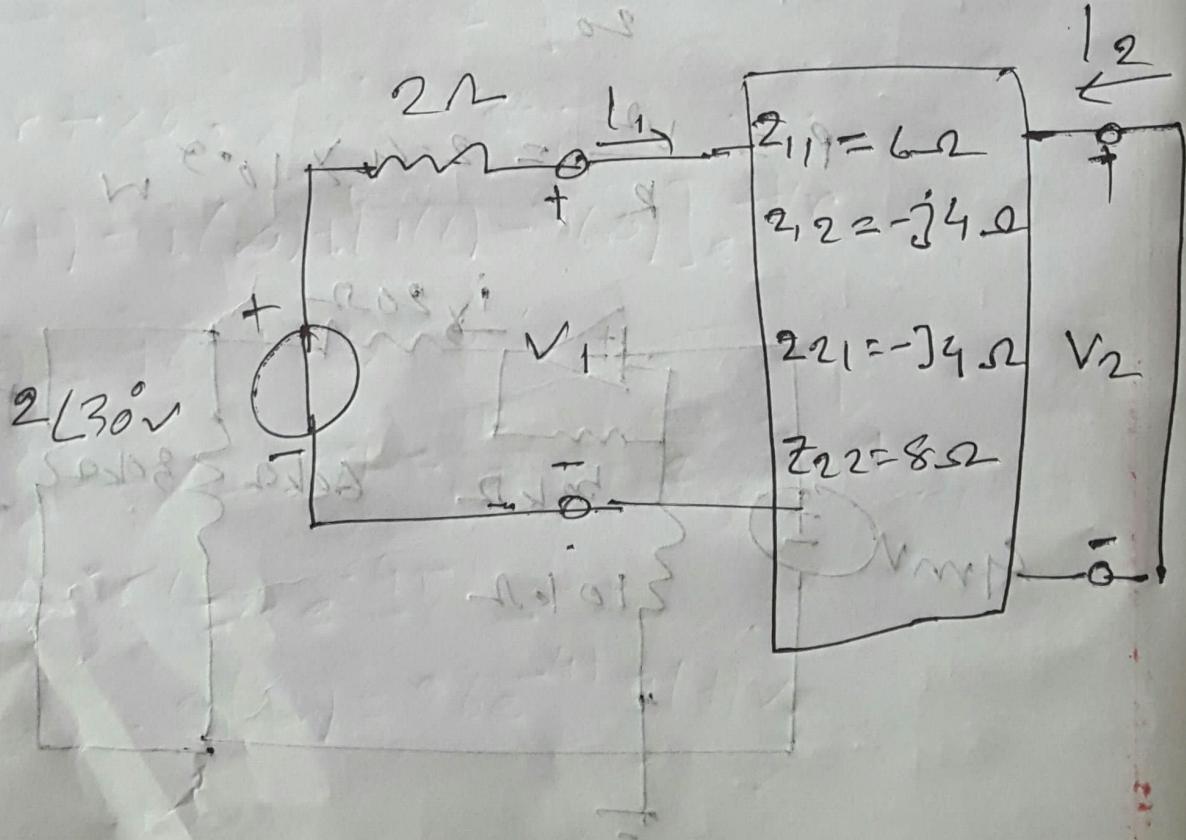
$$\Rightarrow \begin{cases} i_1 = 0.2 \angle 30^\circ A \\ i_2 = 0.1 \angle 120^\circ A \end{cases}$$



Ans. to the Q. No. 6


$$C_{eq1} = \frac{4 \times 12}{4+12} = 3 \mu F$$

$$C_{eq2} = 3 + 3 = 6 \mu F$$


$$C_{eq3} = \frac{6 \times 6}{6+6} = 3 \mu F$$

$$C_{eq4} = 2 + 3 = 5 \mu F$$
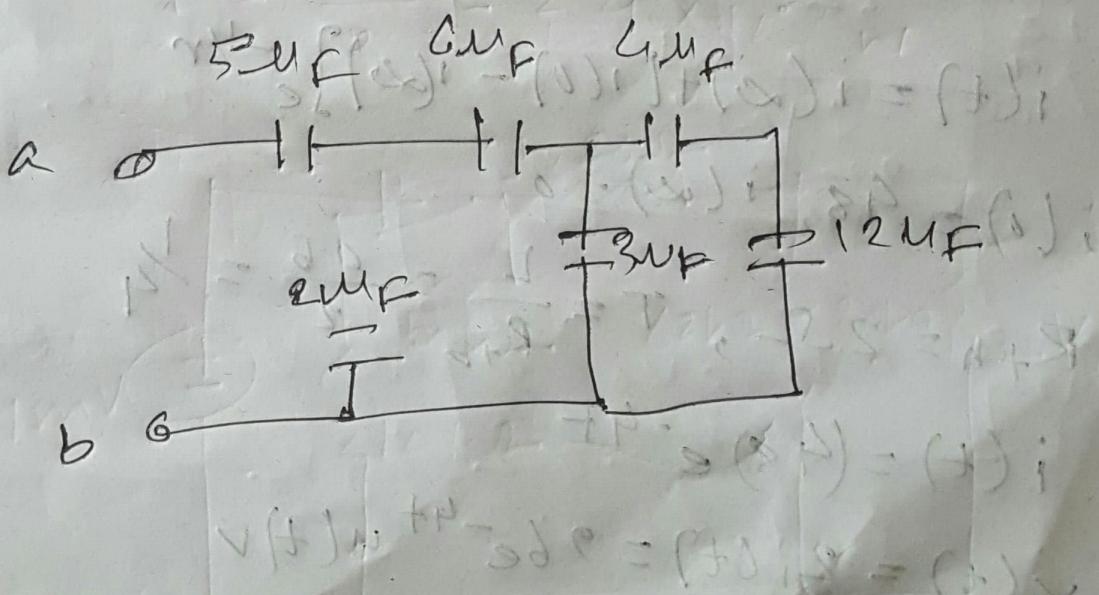
$$C_{eq} = \frac{5 \times 5}{5+5} = 2.5 \mu F$$



(a) Ans. to the Q. No. 9.

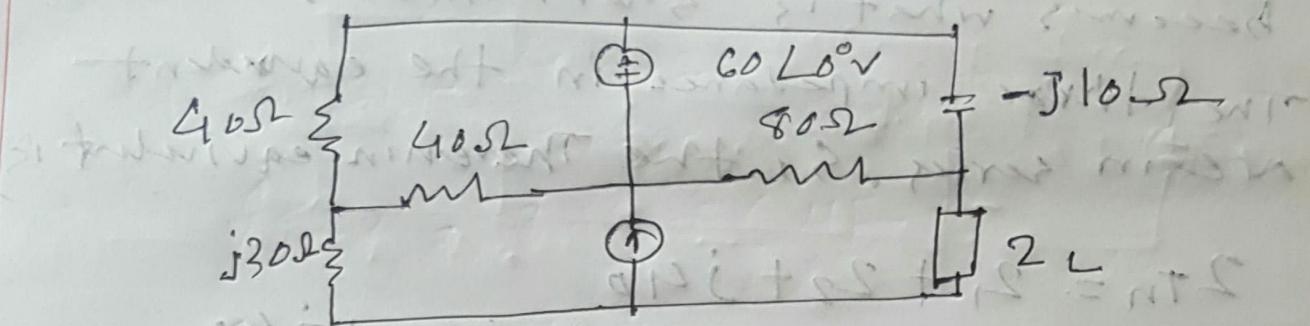

For the circuit shown in fig we need to obtain the value of Z_L .

first we get Thevenin impedance at the load terminals. To get Z_{TH} , we set the independent sources to zero as shown in (a). The $-j10\angle-90^\circ$ capacitor and the 80Ω resistor are in parallel thus,

$$Z_1 = \frac{-j10 \cdot 80}{-j10 + 80}$$

$$= 1.231 - j9.846 \Omega$$

similarly the two 40Ω resistor are in parallel so,

$$Z_2 = 40 \parallel 40 = \frac{40}{20} = 20 \Omega$$


Therefore the circuit shown below in (a) becomes what is shown in (b).

The three impedances in the equivalent are in series. So the Thvenin equivalent is,


$$Z_{Th} = Z_1 + Z_2 + j40$$

$$= 1.231 - j9.846 + 20 + j40$$

$$= 21.231 + j30.154 \Omega$$

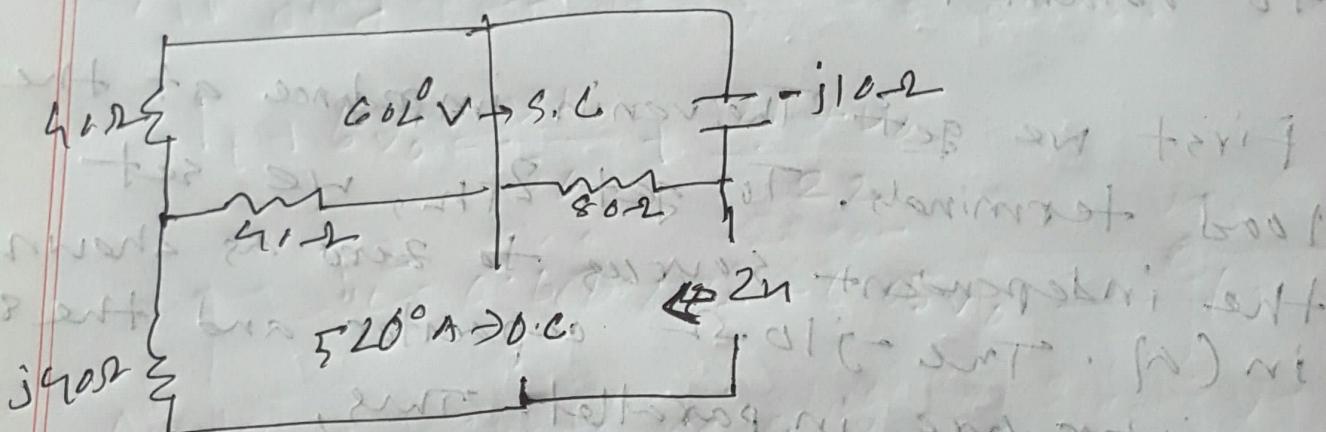

(a)

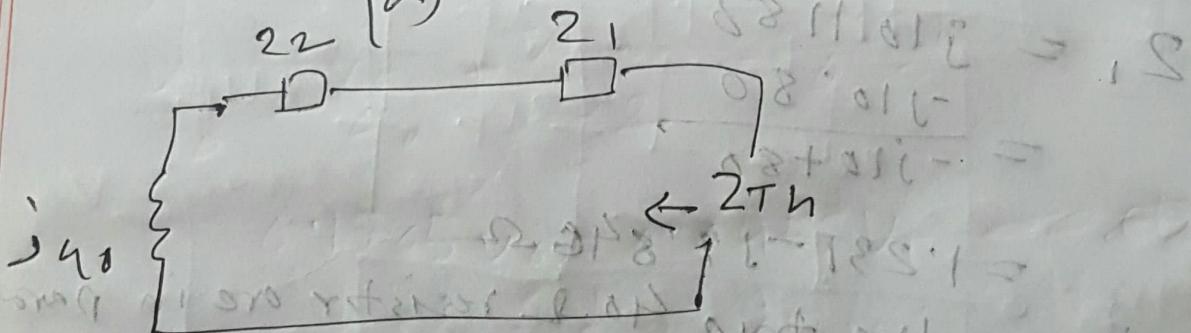

$$(b) \quad Z_{Th} = \frac{60}{20} = 0.15 \Omega = j5 \Omega$$

According to the maximum average power transfer theorem for the sinusoidal steady state, the load impedance draws the maximum power from the circuit when,

$$Z_L = Z_{TH} = 21.231 - j30.154 \Omega$$

\therefore The load impedance for maximum power transfer is $Z_L = 21.231 - j30.154 \Omega$

$$\frac{4-j5V}{5\Omega} + \frac{jV}{5\Omega} = \sqrt{3} \angle 60^\circ$$

$$(1) \rightarrow \sqrt{3} \angle 60^\circ - j\sqrt{3} \angle 60^\circ = 3j$$

current (i.v) 3A & voltage of 33V across 9Ω

$$I = \frac{3A}{9\Omega} = \frac{1V}{3\Omega} + \frac{3V}{9\Omega} + \frac{-1V}{3\Omega}$$

$$(2) \rightarrow 1V \angle 0^\circ + 3V \angle 0^\circ = 4V \angle 0^\circ$$

$$(3) \rightarrow 3V \angle 0^\circ + 3V \angle 0^\circ = 6V \angle 0^\circ$$

$$Z_L = \frac{6V \angle 0^\circ}{3A} = 2\Omega$$