
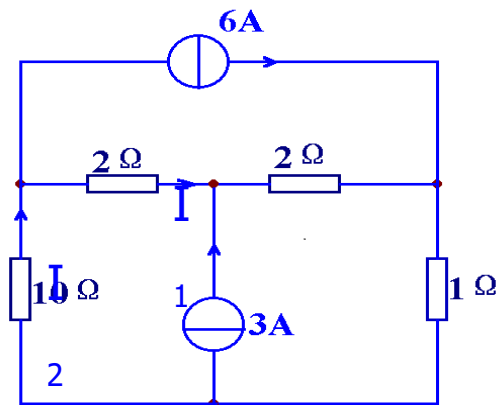


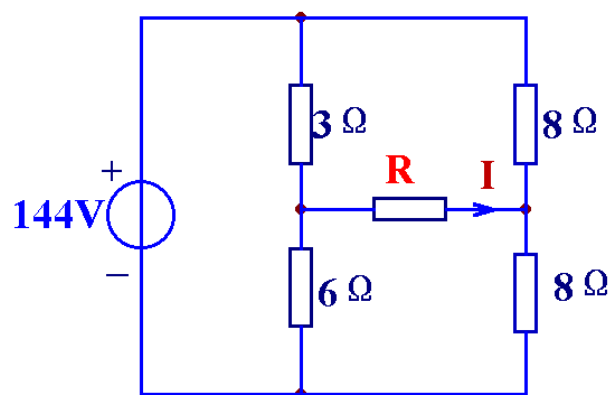
1. Find the current  $I_1$  and  $I_2$  in the following circuit using nodal analysis or mesh analysis.




2. Find the current  $I$  and the power absorbed by the resistor if (a)  $R=2\Omega$ , (b)  $R=6\Omega$ , (c)  $R=18\Omega$ .



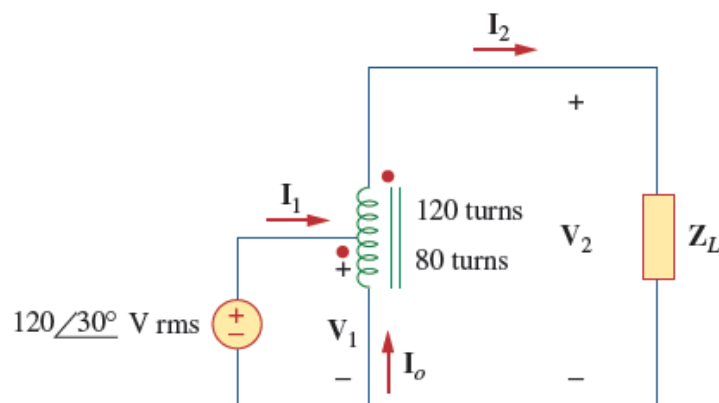3. In the following circuit, calculate: (a)  $I_1$ ,  $I_2$  and  $I_0$  if  $Z_L = 8 + j6\Omega$ , (b) the average power supplied to the load  $Z_L$ .



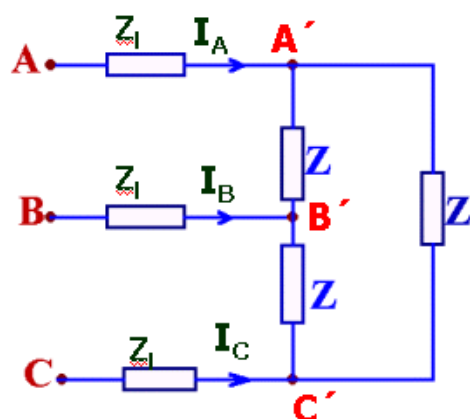4. In the following balanced three-phase circuit, suppose the line voltage  $U_l=380V$ ,  $Z=18+j15\Omega$ ,  $Z_l=3+j4\Omega$ , find the current  $I_A$ ,  $I_B$ ,  $I_C$ .



5. In the following circuit, find the load impedance  $Z_L$  that absorbs the maximum average power. Calculate: (1) the Thevenen equivalent at the load terminals (the subcircuit except  $Z_L$ ), (2) the maximum average power .

