

Name: Samun Islam Ahmed

ID: 2019380182

### Assignment - 6

#### Problem - 3.5

Sol<sup>n</sup>:

$$\begin{array}{r} (i) \quad 00110110 \rightarrow (+54)_{10} \\ + \quad 01000101 \rightarrow (+69)_{10} \\ \hline 01111011 \rightarrow (123)_{10} \end{array}$$

When the result of an arithmetic operation requires  $n+1$  bits, but operating on  $n$ -bit no. then an overflow occurs or If result exceeds the range  $0$  to  $2^{n-1}$  an overflow occurs.

For 8 bits range  $0$  to  $255$

Carry out	Sign bit
0	0
1	1
0	1
1	0

} → No overflow.

→ overflow

→ under

Carry in sign bit = 0

Carry out of sign bit = 0

So No overflow

(ii)

$$\begin{array}{r} 01110101 \rightarrow (117)_{10} \\ (+) 11011110 \rightarrow (222)_{10} \\ \hline 01010011 \rightarrow (339)_{10} \end{array}$$

Carry in sign bit = 1

Carry out of sign bit = 0

No overflow

(iii)

$$00110110 \rightarrow (+54)_{10}$$

$$00101011 \rightarrow (-43)_{10}$$

Binary of 43  $\rightarrow 00101011$

1st Complement  $\rightarrow 11010100$

2nd complement  $\rightarrow +1$  (2's complement)

$$= 11010101$$

$$(+54)_{10} = 00110110$$

$$(-43)_{10} = 11010101$$

$$\begin{array}{r} (+11) = 10001011 \rightarrow \text{mag. representation} \\ \hline \end{array}$$

Carry in sign bit  $\rightarrow 1$

Carry out sign bit  $\rightarrow 1$

No overflow



(iv)  $01110101 \rightarrow (+117)_{10}$   $11001011$  (3)  
(-)  $11010110 \rightarrow (+214)_{10}$   $00101000$  (7)

(-) 11010110  $\rightarrow$  (+214)<sub>10</sub>      00101000 (+7)

Binary of  $214 = 11010110$

1st complement  $\rightarrow 00101001$

2's Complement  $\rightarrow$  11010110

$$-214 = 00101010$$

$$01110101 \rightarrow (+117)_{10}$$

$$00101010 \rightarrow (-214)_{10}$$

$$10011111 \rightarrow -(97)_{10}$$

Carry in sign bit  $\rightarrow 1$

carry out of sign bit  $\rightarrow 0$

overflow

(v)  $11010011 \rightarrow (+211)_{10}$

(-) 11101100  $\rightarrow (-236)_{10}$

Binary of 226  $\rightarrow$  11101100

2's Complement  $\rightarrow 00010011$

29  $\rightarrow$  11 10 1 1 0 0

$$(-236) = 00010100$$

(3)  $11010011 \rightarrow (+21)_{10}$  (4)  
 (+)  $00010100 \rightarrow (+236)_{10}$   


---

 $11100111 \rightarrow -(25)_{10}$

Carry in sign bit = 0

Carry out u u = 0

No overflow

(vi)  $11011111 \rightarrow (222)_{10}$

(+)  $10111000 \rightarrow (184)_{10}$

$10010111 \rightarrow (407)_{10}$   
 magnitude rep.      Remainder in sign

Carry in sign bit  $\rightarrow 1$

Carry out u u  $\rightarrow 1$

No overflow

Problem - 3.7

Soln:

Fig. 2.3(a)  $\rightarrow$

$C_i$	$x_i$	$y_i$	$Count = C_{i+1}$	$S_i$	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	2
0	1	1	1	0	3
1	0	0	0	1	4
1	0	1	1	0	5
1	1	0	1	0	6
1	1	1	1	1	7



④

$x_i y_i$	00	01	11	10
$C_i$	0	1	0	1
$C_i$	1	0	1	0

⑤

$AB = x_i y_i$	00	01	11	10
$C_i$	0	0	1	0
$C_i$	1	1	0	1

SOP

$$S_i = x_i \oplus y_i \oplus C_i \quad \text{--- (i)}$$

$$C_{out} = x_i C_i + x_i y_i + y_i C_i$$

$$= x_i y_i + x_i C_i + y_i C_i$$

$$= x_i y_i + C_i (x_i \oplus y_i) \quad \text{--- (ii)}$$

Again, we use the k-map,


$x_i y_i$	00	01	11	10
$C_i$	0	0	1	0
$C_i$	1	1	1	1

New,  $C_{out} = x_i y_i + \bar{x}_i y_i C_i + x_i \bar{y}_i C_i + 1 \cdot C_i$

$$= x_i y_i + C_i (\bar{x}_i y_i + x_i \bar{y}_i)$$

$$\therefore C_{out} = x_i y_i + C_i (x_i \oplus y_i)$$


5

 

(shown)
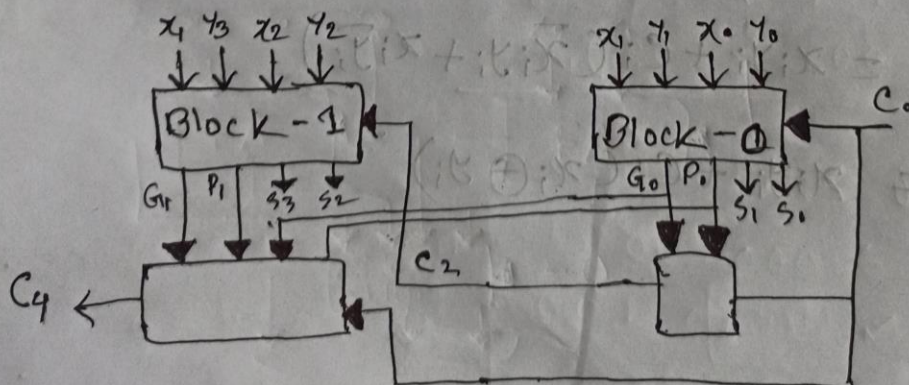
### Problem - 3.14

Sol<sup>n</sup>: The circuits for a 4-bit version of the adder on the hierarchical structure in Fig: 3.17 is constructed as follows:





Block 0 & 1 the structure to the circuit in Fig 3.17. The overall circuit is given by the expression,

$$P_1 = x_1 + y_1$$

$$G_1 = x_1 y_1$$

$$P_0 = P_1 P_0$$

$$G_0 = G_1 + P_1 G_0$$

$$P_1 = P_3 P_2$$

$$G_1 = G_3 + P_3 G_2$$


$$C_2 = G_0 + P_0 C_0$$

$$C_4 = G_1 + P_1 G_0 + P_1 P_0 \cdot C_0$$

Problem - 3.21

Soln: A full adder circuit can be used such that two of bits of the number are connected as inputs 'x' and 'y', while the third bit is connected as carry-in. Then, the carry-out & sum bit will be indicate how many input bits are equal to 1.

(7)

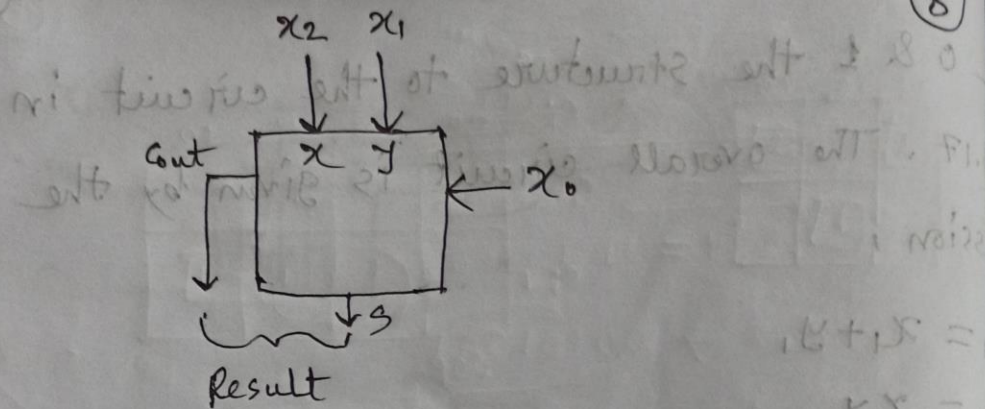

(8)

### Problem - 3.22

Soln: A full adder circuit can be used, such that four bits of input  $x_5, x_4$  in one side & another side  $x_2 \& x_1$ . While there we have two carry-in region  $x_0 \& x_3$  respectively. Then, output coming out from two full adder is connected with 2-bit adder. Now, the carry out & sum bit will indicate how many input bits are equal to 1.

