

05 Resonance

Build a series RLC circuit, keep the output voltage value of AC source unchanged, and adjust frequency of the source signal.

A Report By

Kibria Golam





2019380163

1. When current of resistor reaches maximum I_{\max} , the resonance frequency is found. When current of resistor reaches $0.707I_{\max}$ the half power frequency is found.

Table 1

$R=5\text{-ohm}$, $L=30\text{mH}$, $C=1\mu\text{F}$

f/Hz			f1	896.463	f0	909.726	f2	922.988	
Ir/A			i1	0.072	i0	0.412	i2	0.284	

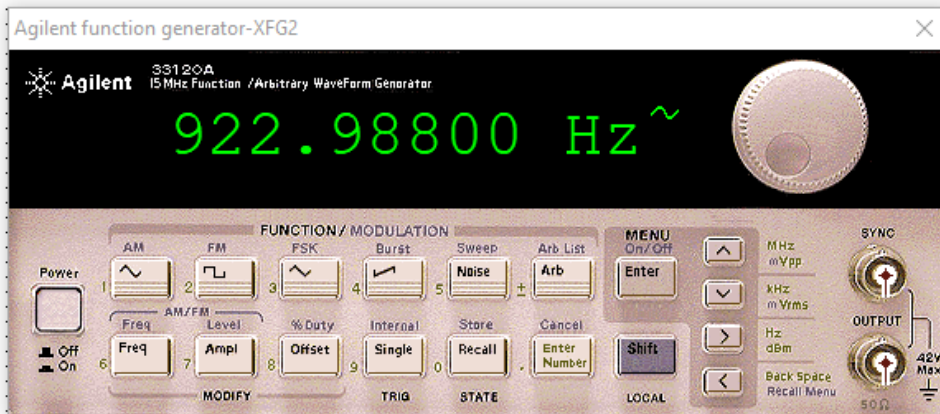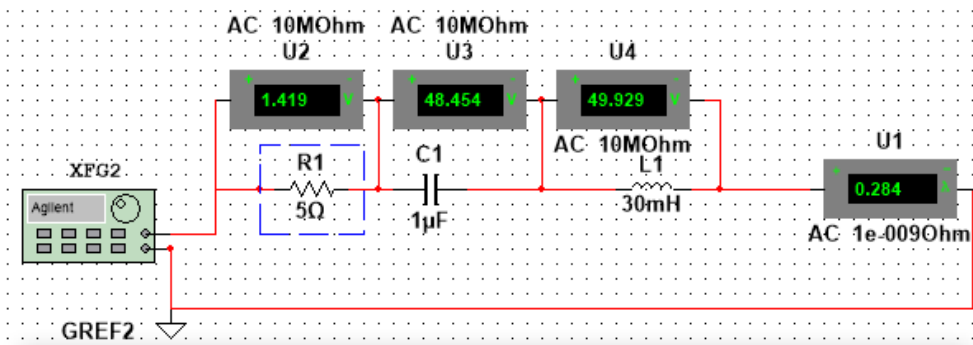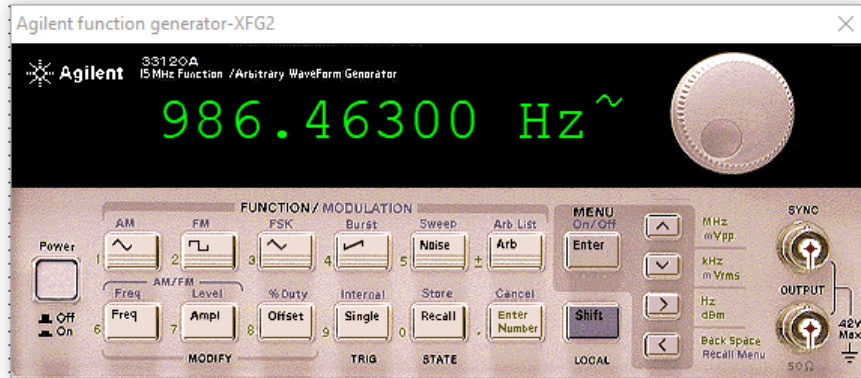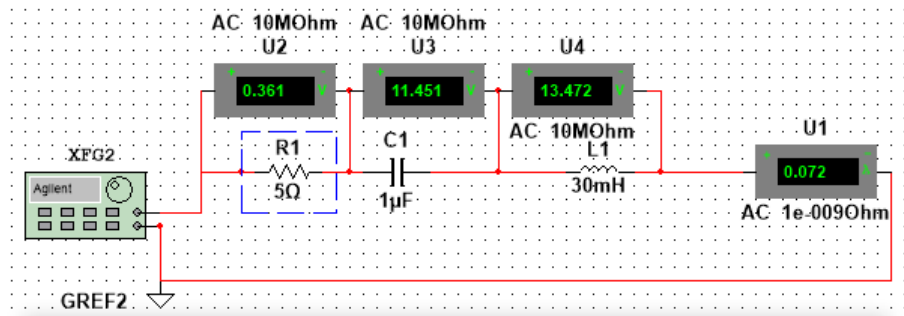


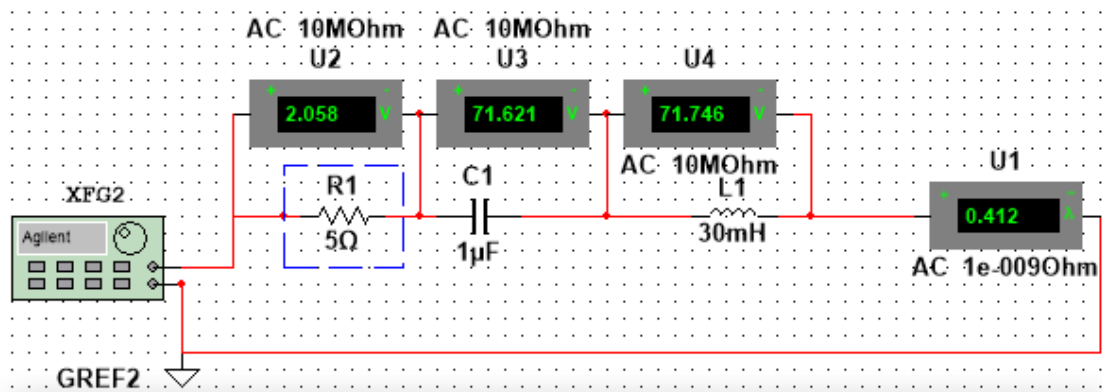


Table 2

$R=50\text{-ohm}$, $L=30\text{mH}$, $C=1\mu\text{F}$

f/Hz			f1	786.37	f0	919	f2	1051.63	
Ir/A			i1	0.029	i0	0.041	i2	0.029	

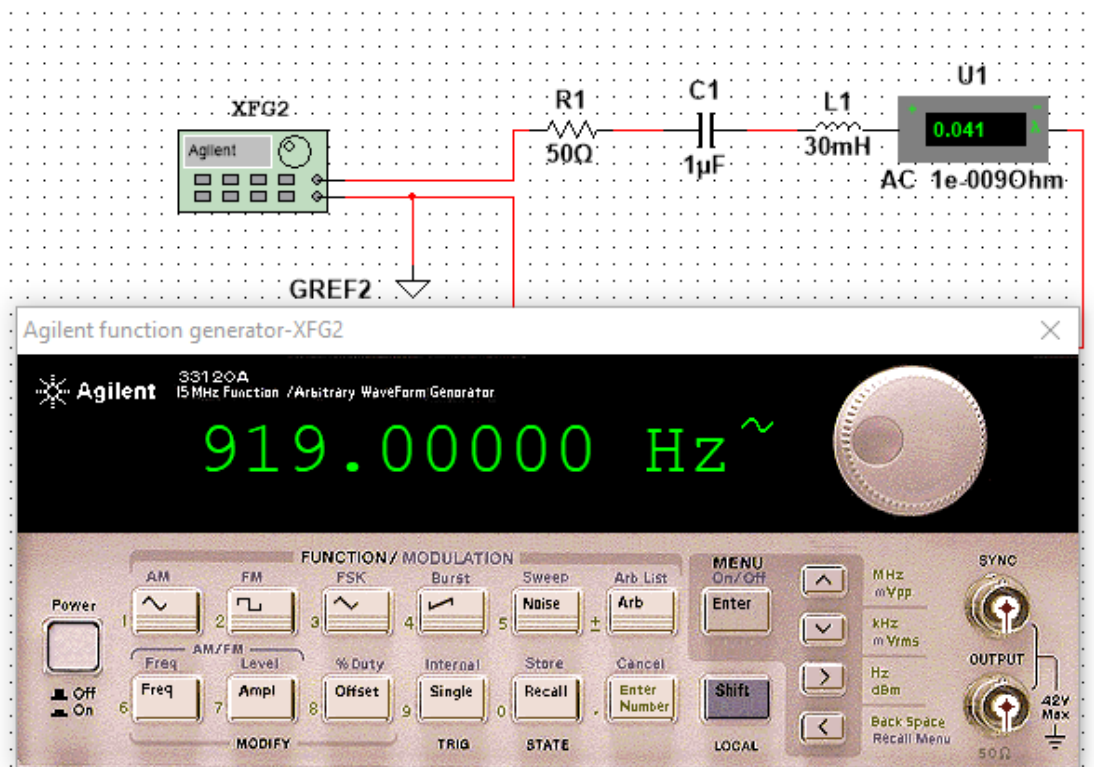


2. When voltage of resistor reaches maximum U_{\max} , the resonance frequency is found. When current of resistor reaches $0.707I_{\max}$ the half power frequency is found.

Table 3

$R=5\text{-ohm}$, $L=30\text{mH}$, $C=1\mu\text{F}$

f/Hz			f1	892.826	f0	906.089	f2	919.351	
Ur/A			U1	0.377	U0	2.016	U2	1.623	

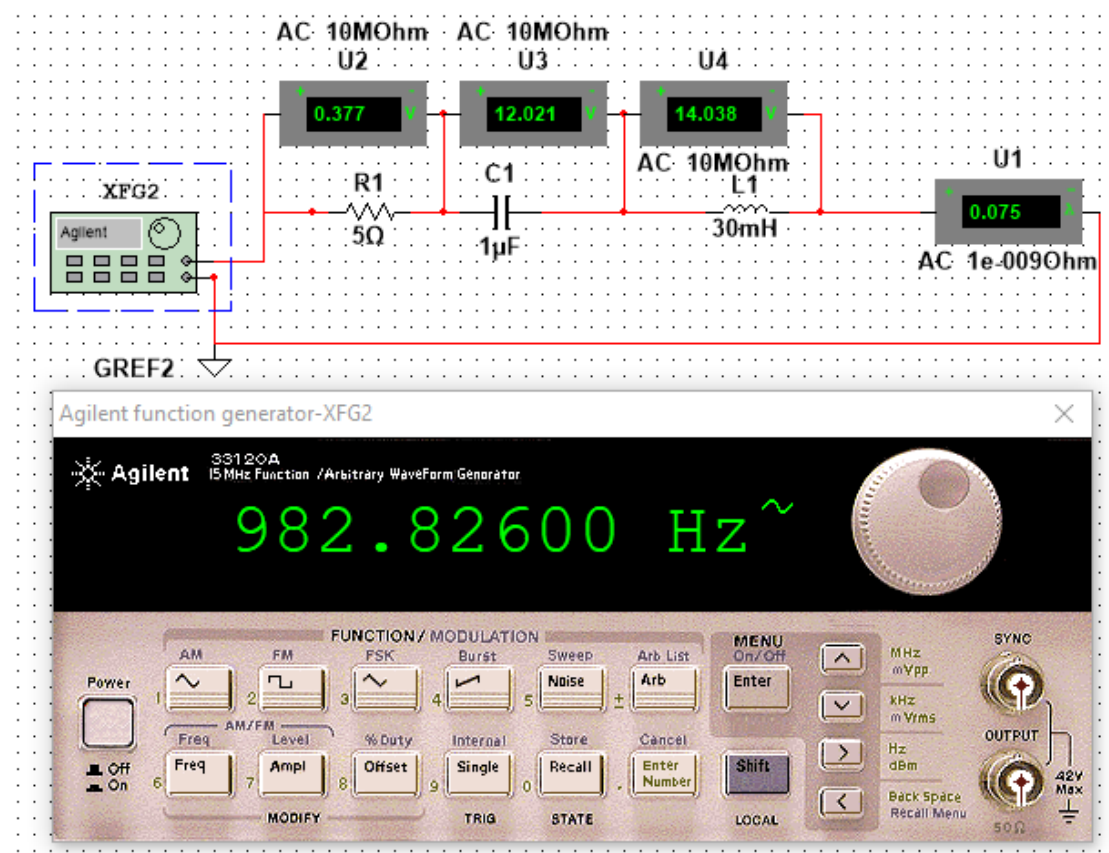


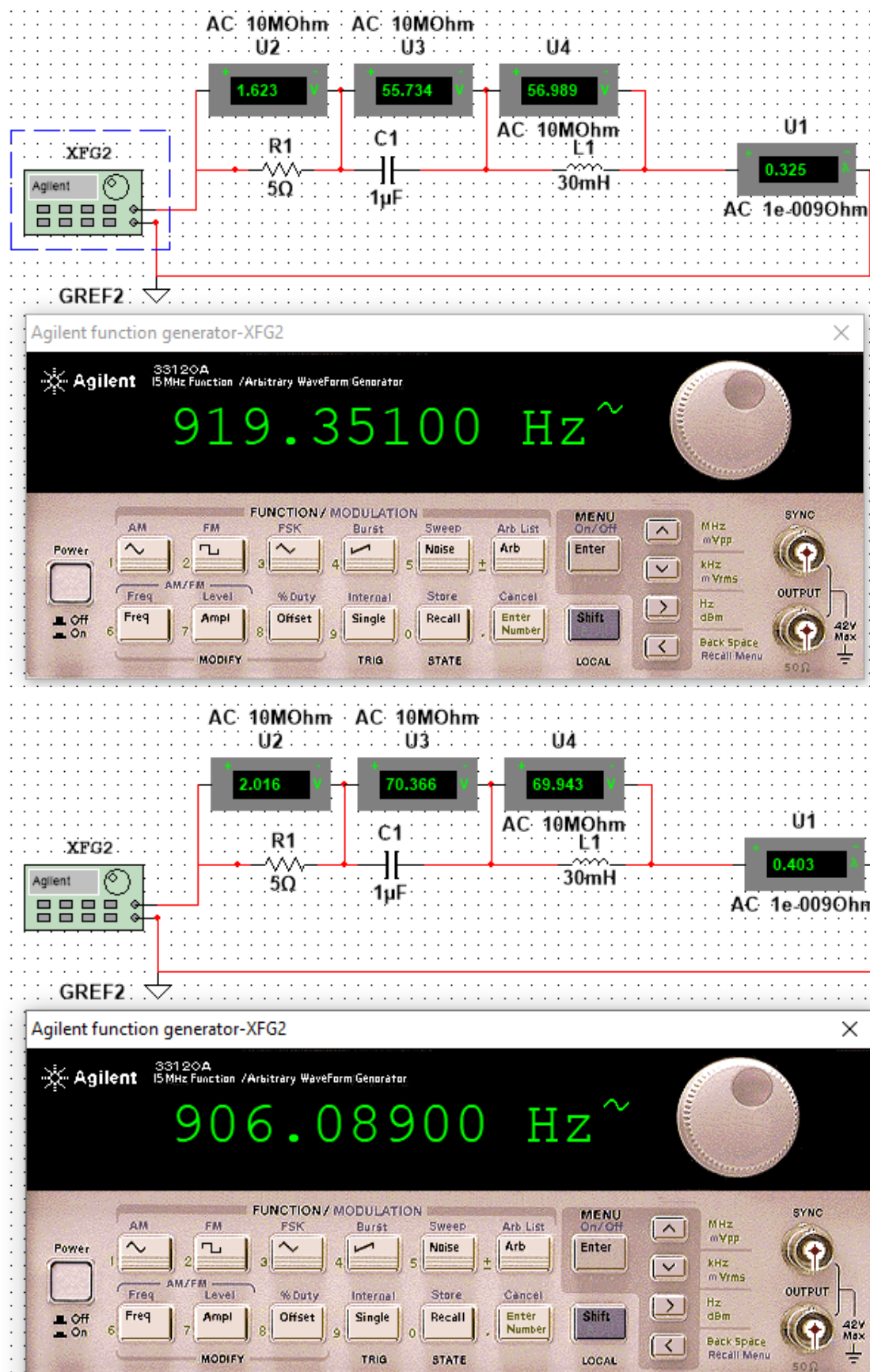


Table 4

$R=50\text{-ohm}$, $L=30\text{mH}$, $C=1\mu\text{F}$

f/Hz			f1	786.37	f0	919	f2	1051.63	
Ur/A			U1	1.464	U0	2.057	U2	1.453	

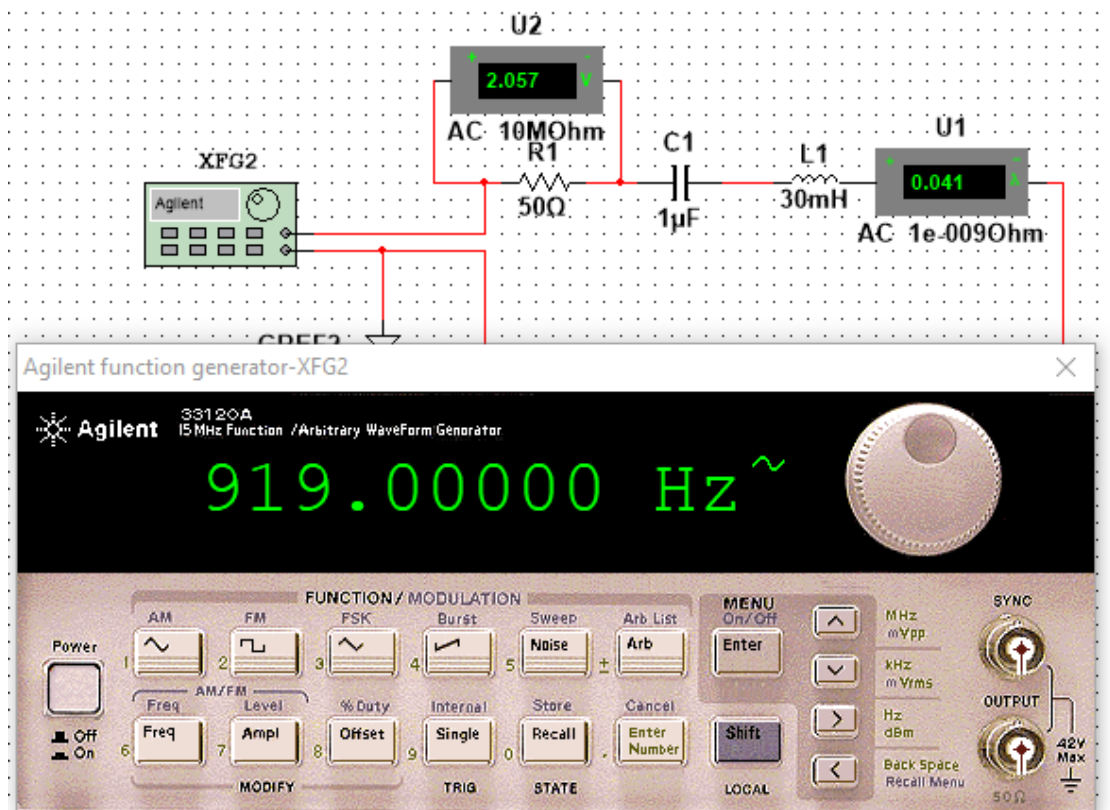


3. When voltage values on inductor and capacitor are the same, the resonance frequency is found. Record maximum voltage U_{max} on resistor, then found half power frequency.

Table 5

$R=5\text{-ohm}$, $L=30\text{mH}$, $C=1\mu\text{F}$

f/Hz			f_1	890.989	f_0	904.252	f_2	917.514	
I_R/A			I_{R1}	0.243	I_{R0}	0.389	I_{R2}	0.346	
U_R/V			U_{R1}	1.216	U_{R0}	1.943	U_{R2}	1.731	
U_L/V			U_{L1}	41.243	U_{L0}	67.218	U_{L2}	60.752	
U_C/V			U_{C1}	42.858	U_{C0}	67.892	U_{C2}	59.647	

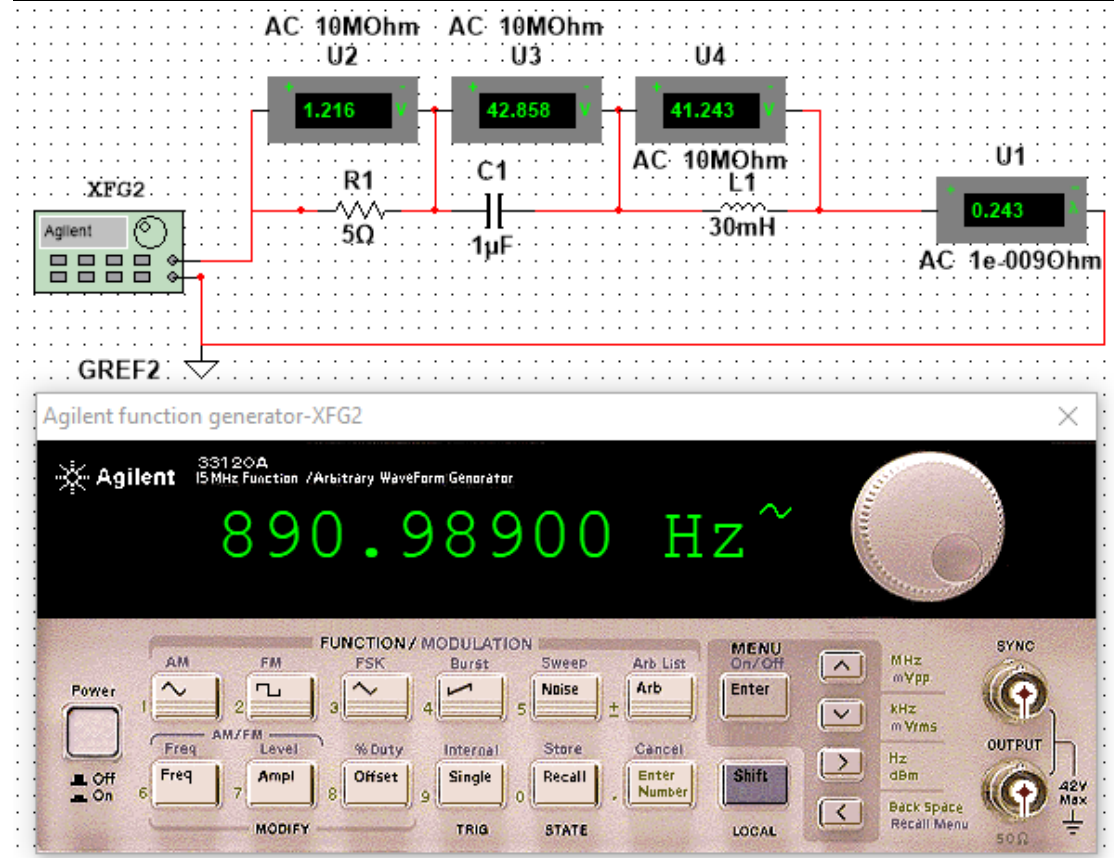


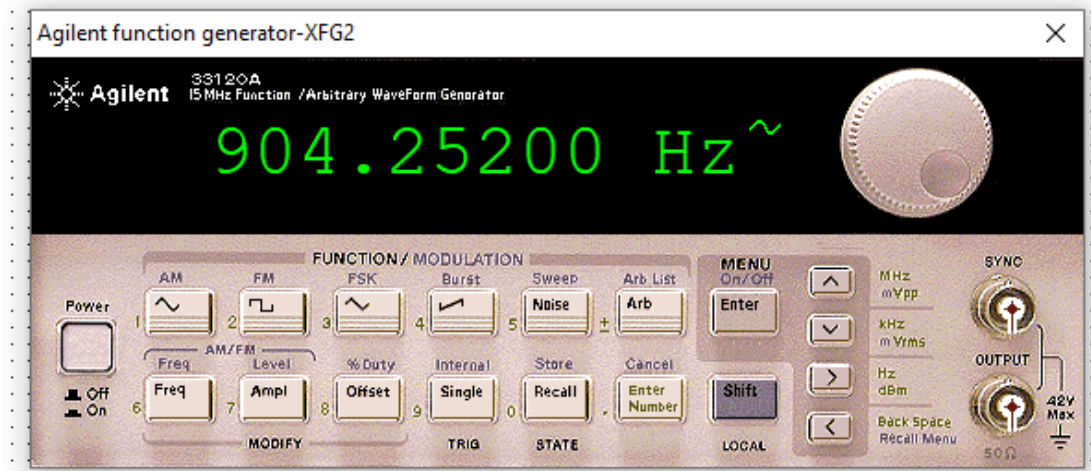
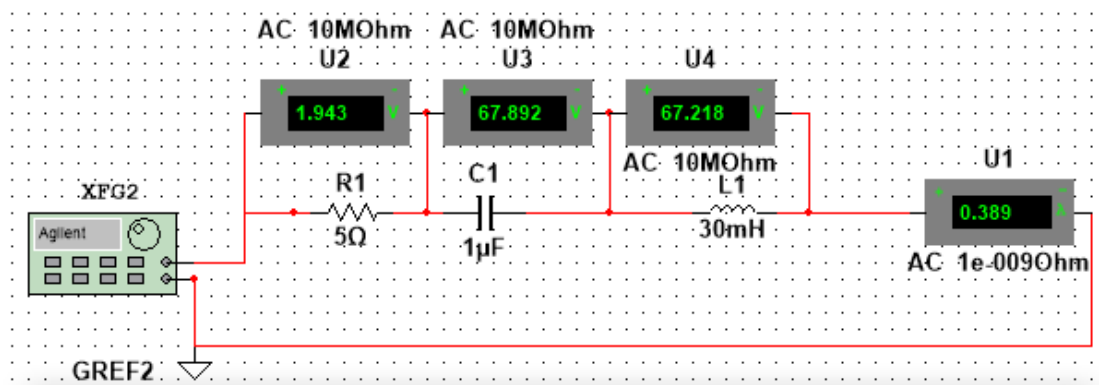
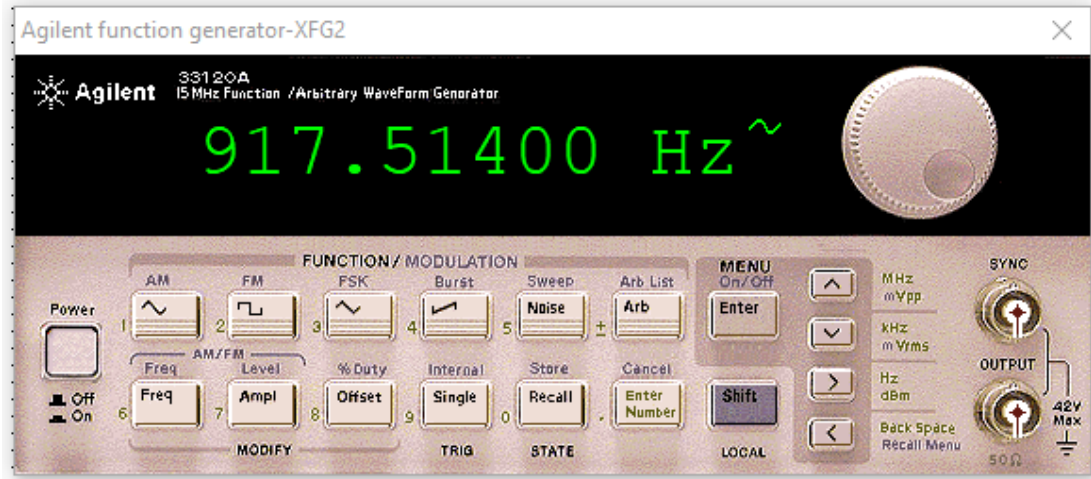


Table 6

$R=50\text{-ohm}$, $L=30\text{mH}$, $C=1\mu\text{F}$

f/Hz			f ₁	771.28	f ₀	903.91	f ₂	1036.53	
I _R /A			I _{R1}	0.027	I _{R0}	0.041	I _{R2}	0.031	
U _R /V			U _{R1}	1.37	U _{R0}	2.062	U _{R2}	1.527	
U _L /V			U _{L1}	4.203	U _{L0}	7.222	U _{L2}	6.099	
U _C /V			U _{C1}	5.574	U _{C0}	7.223	U _{C2}	4.65	

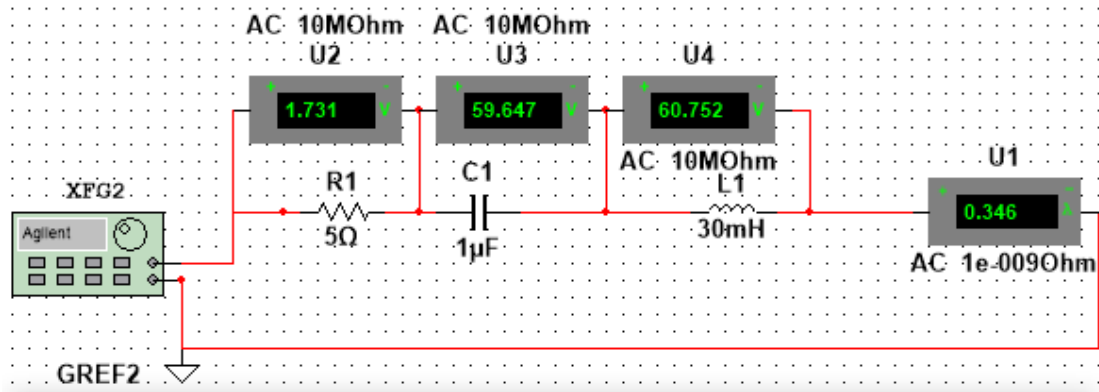