

Name: Samun Islam Ahmed


①

ID: 2019380182

Assignment - 7

Problem - B.1

Soln: a)

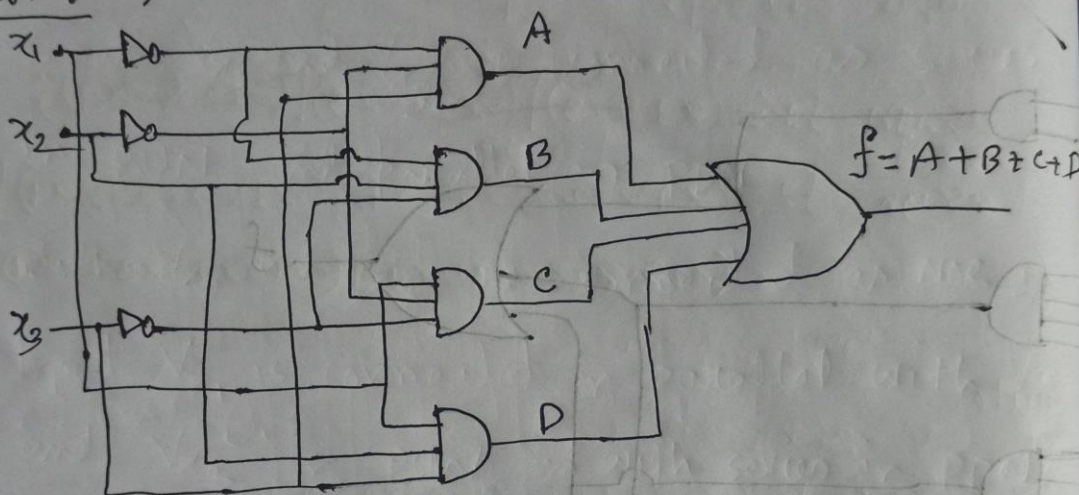

$$A = \bar{x}_1 \bar{x}_2 x_3$$

$$B = \bar{x}_1 x_2 \bar{x}_3$$

$$C = x_1 \bar{x}_2 \bar{x}_3$$

$$D = x_1 x_2 x_3$$

x_1	x_2	x_3	A	B	C	D	$f = A + B + C + D$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1
0	1	0	0	1	0	0	1
0	1	1	0	0	0	0	0
1	0	0	0	0	1	0	1
1	0	1	0	0	0	0	0
1	1	0	0	0	0	0	0
1	1	1	0	0	0	1	1

(2)

b) From part (a), There are 3 NOT gates. So $3 \times 2 = 6$ transistors need to build 3 NOT gates.
There are 4 3 input AND gates which requires 8 transistors.

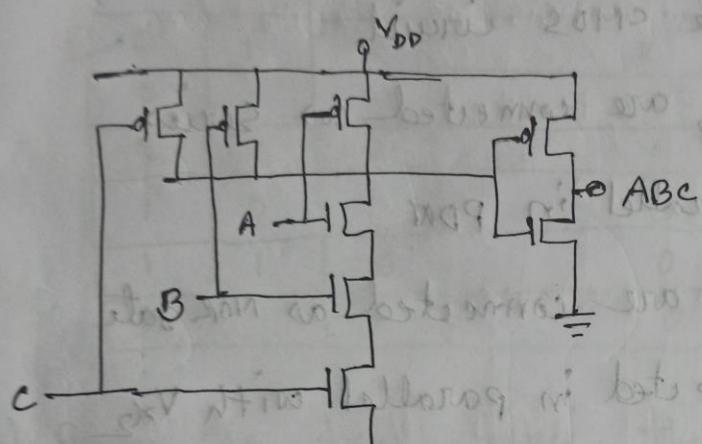


Fig: 4-3 input AND gates requires 8 Transistors

Therefore 4 3-input AND require $4 \times 8 = 32$ transistors
and 4-input OR gate requires 10 transistors.

Gate	NOT	3-input AND	4-input OR
Number of Gates	3	4	1
Number of Transistors per gate	2	8	10

$\therefore \text{Total number of transistors} = 2 \times 3 + 8 \times 4 + 10 \times 1 = 48$

Problem- B.6

3

Soln^o a) Inputs for the circuit in Figure PB.4

are V_{x1}, V_{x2}, V_{x3} and output is V_f

Let us consider the CMOS circuit,

- Inputs V_{x2} and V_{x3} are connected as series in PUN and parallel in PDN
- Both V_{x2} and V_{x3} are connected as NOR gate
- Input V_{x1} is connected in parallel with V_{x2} and V_{x3} in PUN and with series in PDN.

Therefore logical NAND operation is performed with V_{x1} and $(V_{x2} + V_{x3})$

Hence,

$$V_f = \overline{V_{x1} \cdot (V_{x2} + V_{x3})}$$

$$= \overline{V_{x1}} + \overline{V_{x2} + V_{x3}}$$

$$= \overline{V_{x1}} + \overline{V_{x2}} \cdot \overline{V_{x3}}$$

Truth Table

(4)

V_{x_1}	V_{x_2}	V_{x_3}	$V_f = \overline{V_{x_1}} + \overline{V_{x_2}} \cdot \overline{V_{x_3}}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

b) From the truth table, the canonical sum-of-products expression can be derived as,

$$V_f = \overline{V_{x_1}} \overline{V_{x_2}} \overline{V_{x_3}} + \overline{V_{x_1}} \overline{V_{x_2}} V_{x_3} + \overline{V_{x_1}} V_{x_2} \overline{V_{x_3}} + \overline{V_{x_1}} V_{x_2} V_{x_3} + V_{x_1} \overline{V_{x_2}} \overline{V_{x_3}} + V_{x_1} \overline{V_{x_2}} V_{x_3} + V_{x_1} V_{x_2} \overline{V_{x_3}} + V_{x_1} V_{x_2} V_{x_3}$$

So we require,

Five 3-input AND gate

Three NOT Gate

5-input OR gate

5

A three-input AND gate need 8 transistors

A NOT gate need 2 transistors.

A five-input OR gate need 12 transistors.

∴ The number of transistors required is

$$= 5 \times 8 + 3 \times 2 + 1 \times 12$$

$$= 40 + 6 + 12$$

$$= 58 \text{ transistors.}$$

Problem - B. 8

Soln: The output of given digital circuit

is,

$$V_f = V_{x_2} + V_{x_1} \cdot V_{x_3}$$

The complement of the output is,

$$\begin{aligned} \overline{V_f} &= \overline{V_{x_2} + V_{x_1} \cdot V_{x_3}} = \overline{V_{x_2}} \cdot \overline{V_{x_1} \cdot V_{x_3}} \\ &= \overline{V_{x_2}} (\overline{V_{x_1}} + \overline{V_{x_3}}) \end{aligned}$$

Therefore the other half of the circuit will be,

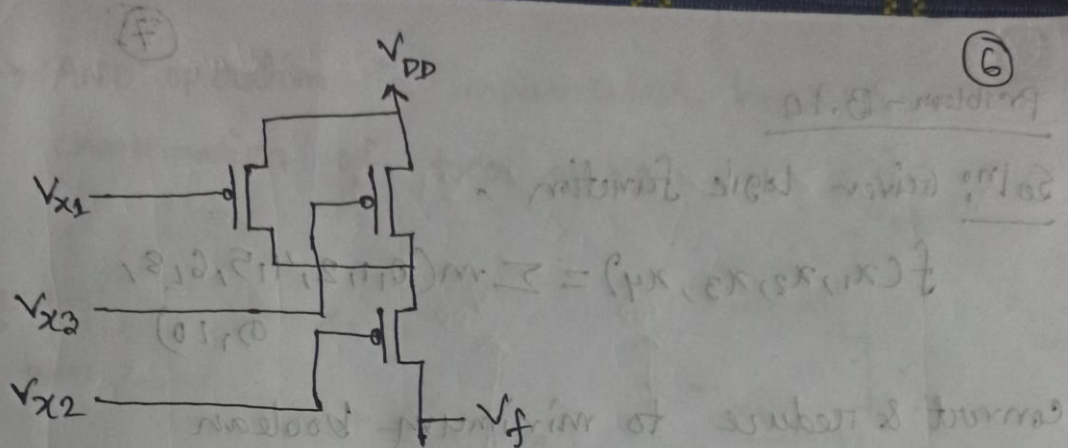


Fig-The other half of the circuit containing only PMOS transistors.

The complete circuit is shown below,

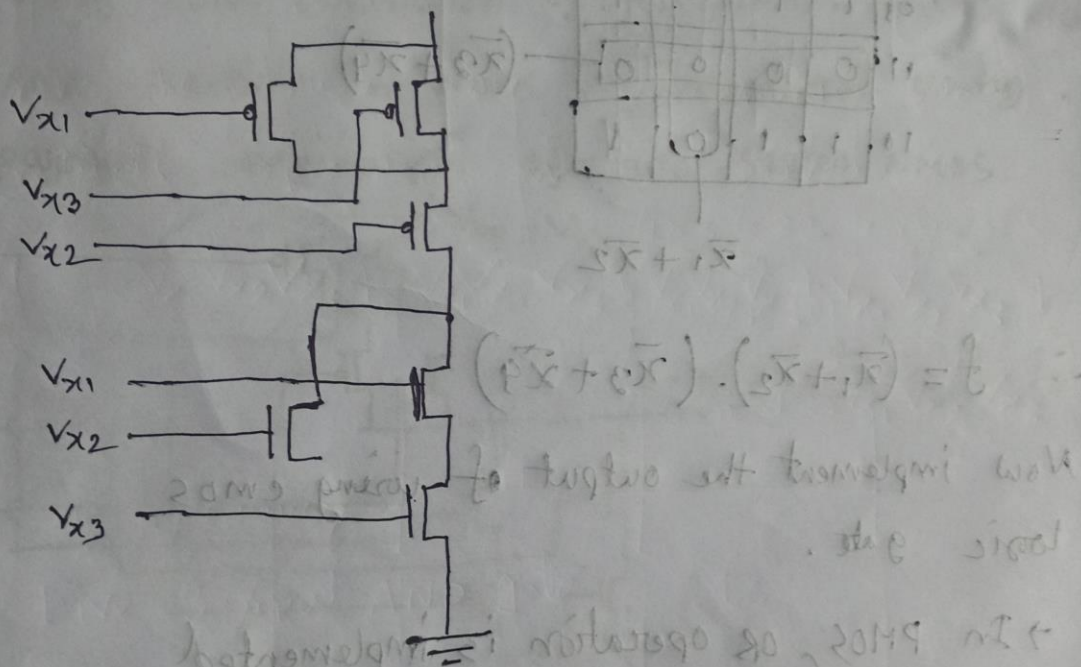



Fig-The complete circuit.

Problem - B.10

Soln: Given logic function

$$f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 10)$$

 convert & reduce to minimum boolean algebra using k-map.




$$\therefore f = (x_1 + x_2) \cdot (x_3 + x_4)$$


Now implement the output of using CMOS logic gate.

→ In PMOS, OR operation is implemented using parallel combination of two PMOS.

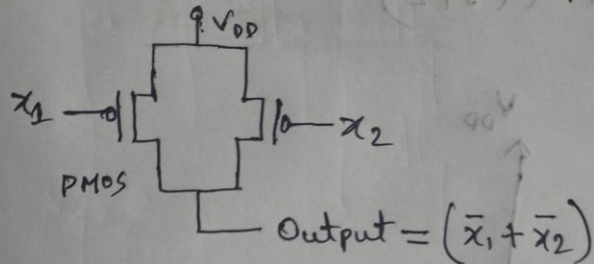→ AND operation is implemented by series combination of two PMOS




parallel combination

 

Series combination

→ In case of NMOS, OR operation is implemented using series combination of two NMOS.

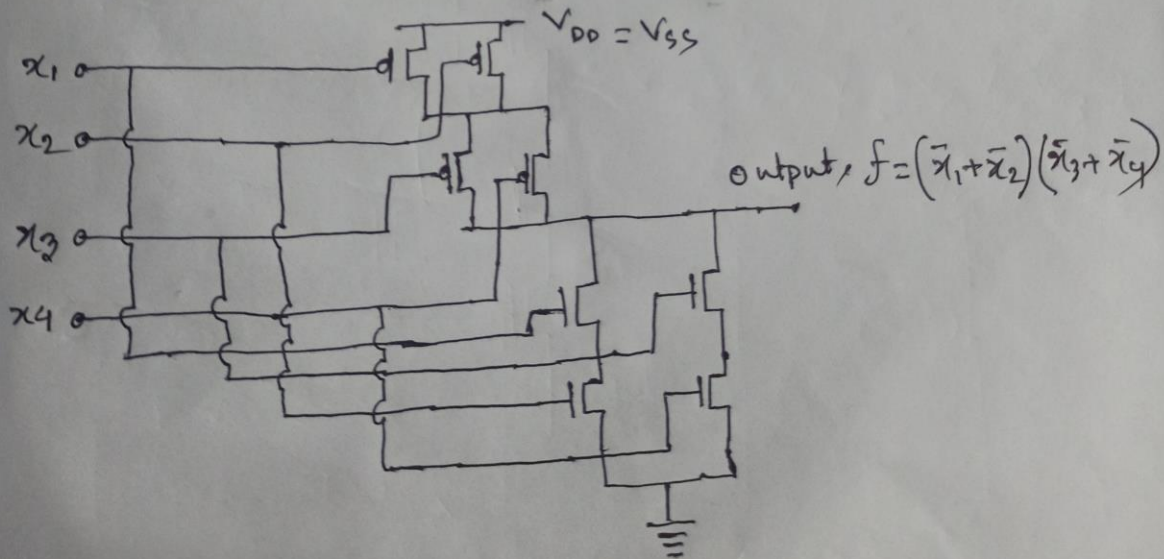→ AND operation in NMOS is implemented using parallel combination of two series NMOS.



8

Problem-B.12

9

Soln: $f = xy + xz + yz$

