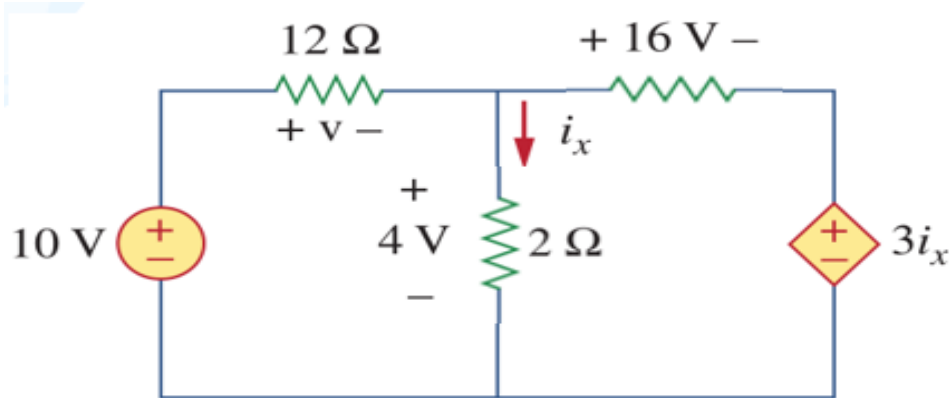


Homework (2th time)

1. Calculate the absorbed power of each resistor and the supplied power of each source in the circuit.



Answer:

For loop 1, $-12 + v + 2 = 0$, $v = 10 \text{ V}$

For loop 2, $-2 + 8 + 3i_x = 0$, $i_x = -2 \text{ A}$

Time up

Answer Sheet
(4/4)

1. (25 scores) Find the power absorbed by each of the elements in Figure 1.

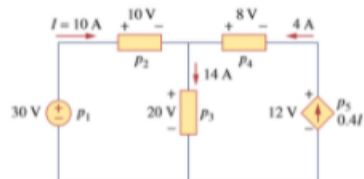


Figure 1

$$P_1 = 30 \times (-10) = -300W$$

$$P_2 = 10 \times 10 = 100W$$

$$P_3 = 20 \times 14 = 280W$$

$$P_4 = 8 \times (-4) = -32W$$

$$P_5 = 12 \times (-0.4 \times 10) = -48W$$

2. (25 scores) Find V_0 and the power absorbed by each of the element in Figure 2.

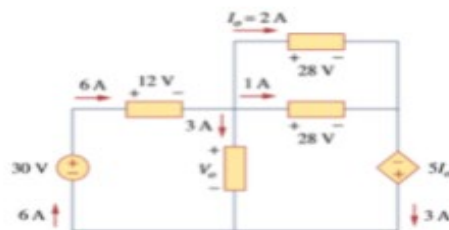


Figure 2

$$V_0 = (30 - 12)V = 18V$$

$$P_1 = 30 \times (-6) = -180W$$

$$P_2 = 12 \times 6 = 72W$$

$$P_3 = 18 \times 3 = 54W$$

$$P_4 = 28 \times 1 = 28W$$

$$P_5 = 28 \times 2 = 56W$$

$$P_6 = 5 I_o \times (-3) = 5 \times 2 \times (-3) = -30W$$

3. (25 scores) Find the power absorbed by each element in the circuit.

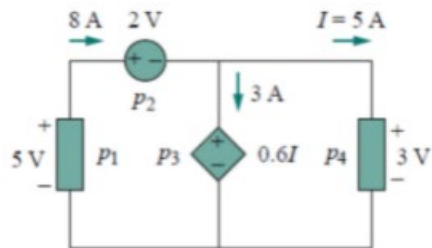


Figure 3

$$\begin{aligned} P_1 &= -40 \text{ W} \\ P_2 &= 16 \text{ W} \\ P_3 &= 9 \text{ W} \\ P_4 &= 15 \text{ W} \end{aligned}$$

Time up

Answer Sheet
(4/4)

4. (25 scores) Determine the power supplied by the dependent sources.

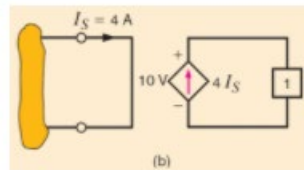
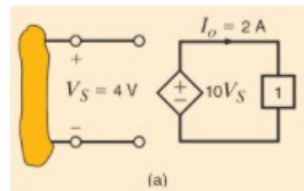


Figure 4

-80 W
160 W