

07 Operational Amplifier

Use op amp to realize the expression below, U1, U2 and U3 are input voltage, and make sure U1, U2 and U3 are variable.

$$U_o = 3u_1 - 7u_2 + 5u_3$$

A Report By

Kibria Golam
ID: 2019380163

- Use op amp to realize the expression below, U_1 , U_2 and U_3 are input voltage, and make sure U_1 , U_2 and U_3 are variable.


$$U_o = 3u_1 - 7u_2 + 5u_3$$

To create the expression $U_o = 3u_1 - 7u_2 + 5u_3$ using op amp, I have created the whole thing by 3 separate op amp.


First, I created 3 circuits with a gain of 2, 7, 5 respectively. For the gain $3u_1$ and $5u_3$, I used non inverting op amp and for the $-7u_2$ part, I used inverting op amp to generate inverse voltage. And finally, I used a non-inverting op amp with a gain of 1 to sum up $3u_1$, $-7u_2$ and $5u_3$ to produce the final output, $U_o = 3u_1 - 7u_2 + 5u_3$.

Steps:

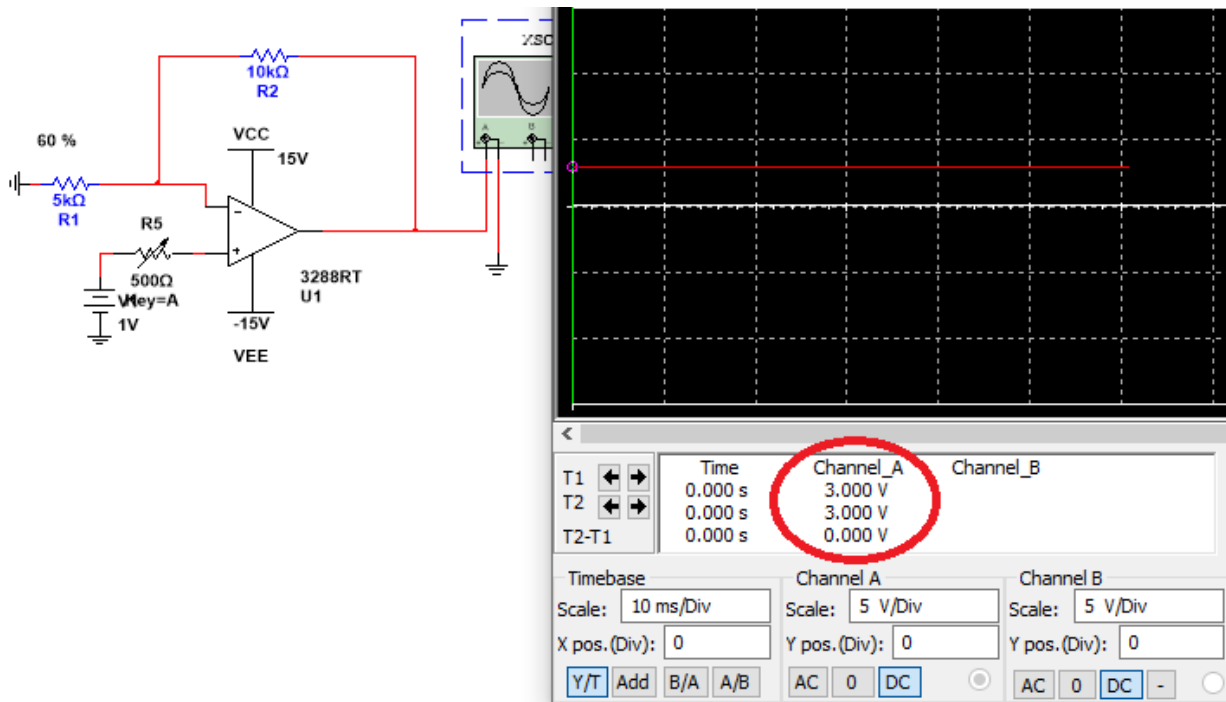
To generate $3u_1$: The source voltage is $u_1=1V$. Thus, the output of the circuit below is $3u_1 = 3V1 = 3 \times 1V = 3V$.



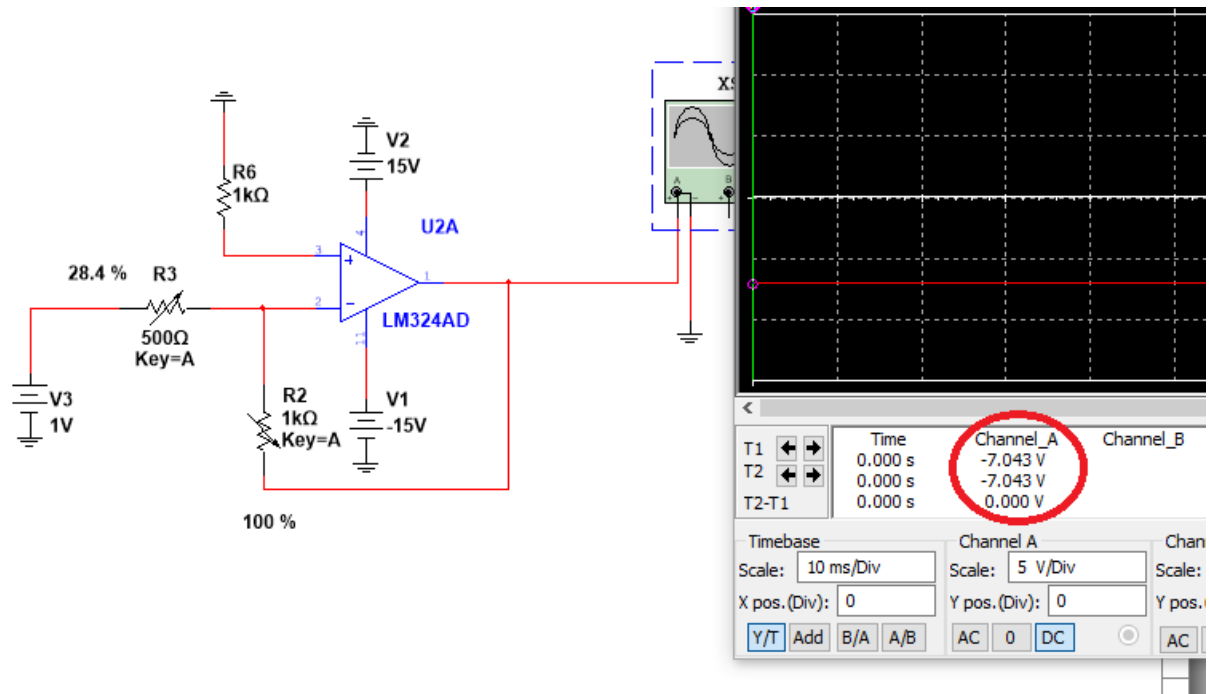To generate $-7u_2$: The source voltage is $u_2 = V_3 = 1V$. Thus, the output of the circuit below is $-7u_2 = -7 \times V_3 = -7 \times 1 = -7V$.




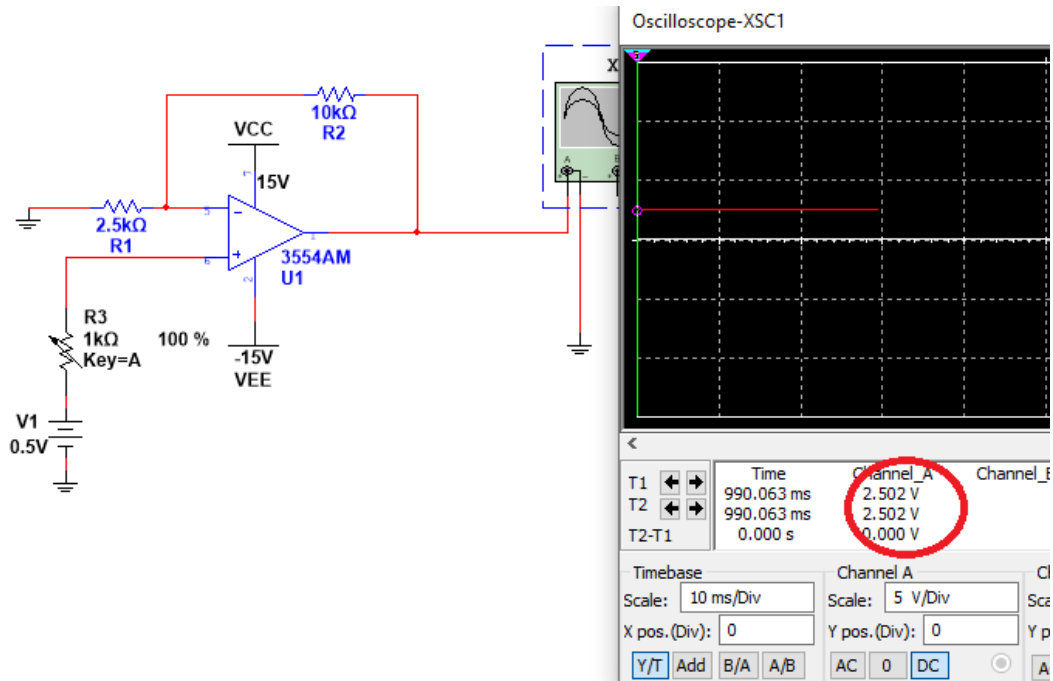To generate $5u_3$: The source voltage is $u_3=0.5$ V. Thus, the output of the circuit below is $5u_1= 5V_1= 5 \times 0.5 =2.5$ V.



And Finally, to generate U_0 :

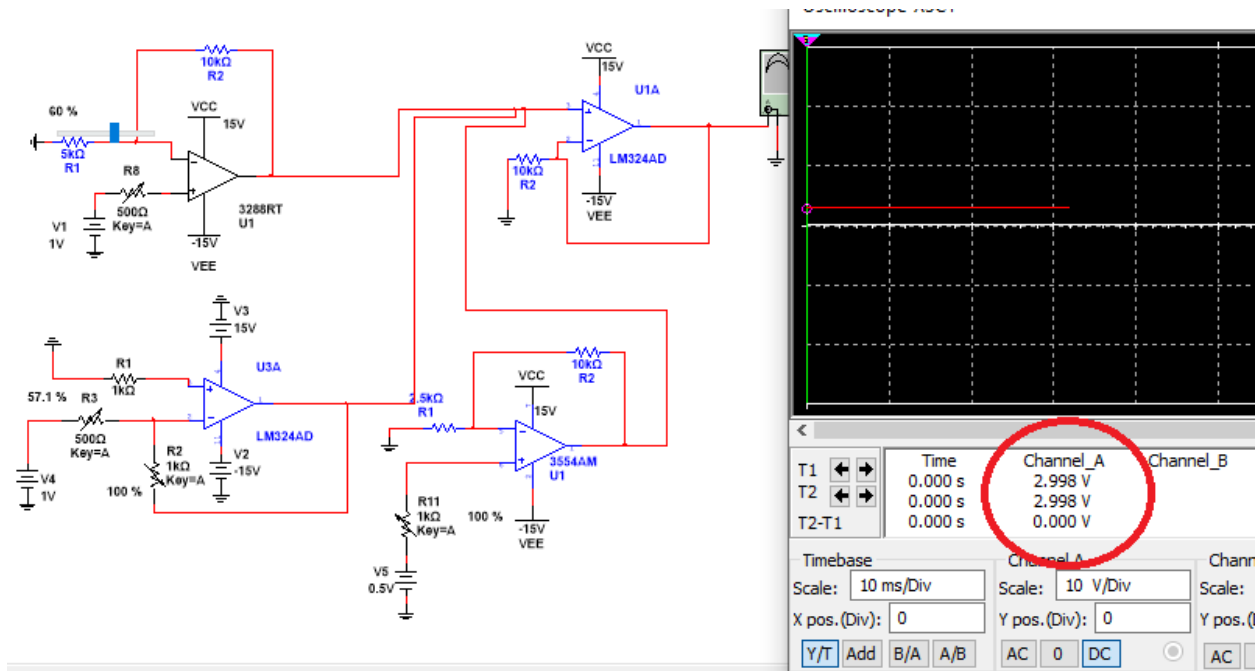By summing up $3u_1$, $-7u_2$ and $5u_3$, the final output, $U_0 = 3u_1 - 7u_2 + 5u_3 = 3V - 7V + 2.5V \approx 3V$.



Appendix:

It was possible to do the whole circuit using a single op amp chip which contains 4 separate op amp inside. But I realized the thing after creating the whole circuit and thought to go on with this.